



Radio Design 401 Episode 1 – Low-power Receivers in Crowded Spectrum Environments (a White Paper)

Slides downloaded from: <https://ecefies.org/>

Companion videos at: <https://www.youtube.com/playlist?list=PL9Ox3wpnB0krNexW2k5JMCaewXN7LoRXd>

This material is provided by ecefies.org for educational use .

This is the first episode in our follow-on to the Radio Design 101 series. In RD401, we will be covering more advanced topics including fundamental research into how to improve the performance of receivers in dense spectrum environments. In keeping with RD101 series, we will be using the FM broadcast band for our demonstrations - but the material and circuit technologies are applicable to all radio receivers.

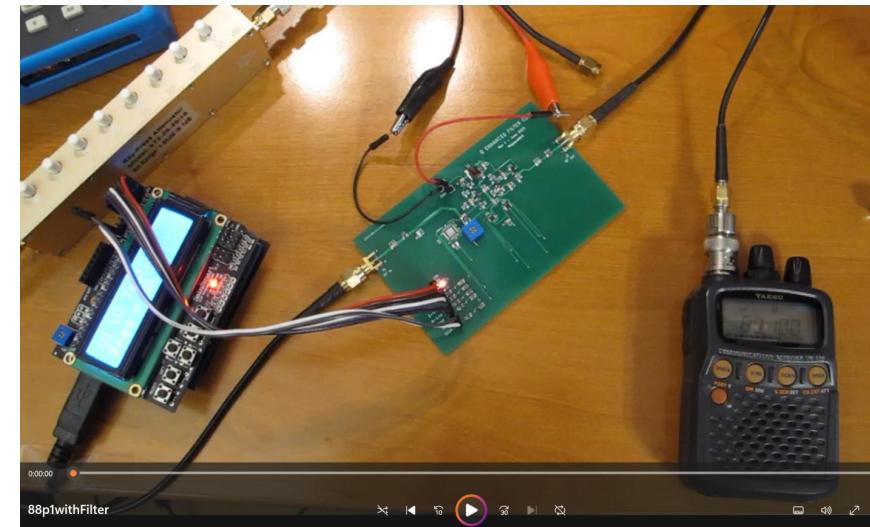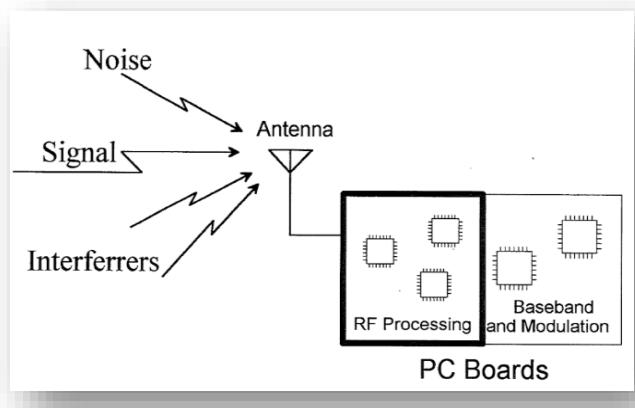




Radio Design 401

Episode 1

*Low-power Receivers in
Crowded Spectrum Environments*

(An Advanced “Course” & “White Paper”)

“Prereq”: Radio Design 101 ☺

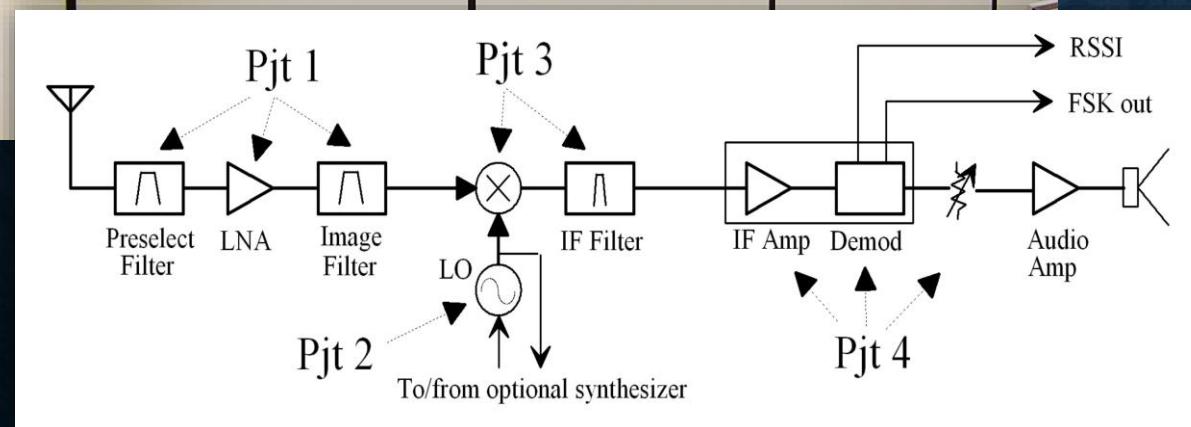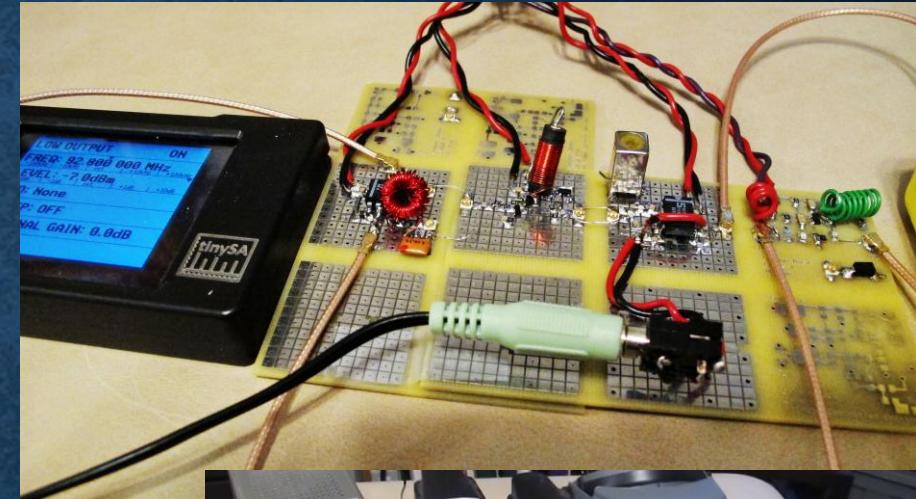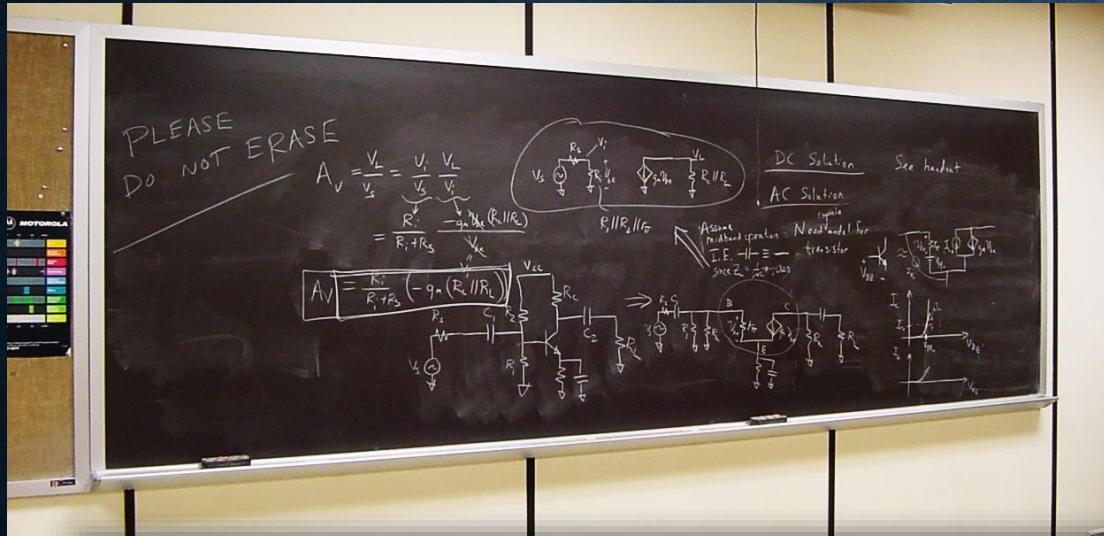

What's a “White Paper”

The image shows a Google search results page. The search query "what is a \"white paper\"" is entered in the search bar. Below the search bar, there are navigation links: All, Images, Videos, Shopping, Forums, Web, News, and More. A blue star icon followed by the text "AI Overview" is present. The main content is a snippet from an AI-generated response: "A \"white paper\" is an informative document, often used in business, that presents a detailed analysis of a specific topic, problem, or solution, usually with the intent to educate the reader and persuade them to support a particular viewpoint or product, often by providing facts and evidence in a professional and authoritative tone; the term originated from". The text is displayed in a white box with a thin black border.



what is a "white paper"

All Images Videos Shopping Forums Web News More

AI Overview



A "white paper" is an informative document, often used in business, that presents a detailed analysis of a specific topic, problem, or solution, usually with the intent to educate the reader and persuade them to support a particular viewpoint or product, often by providing facts and evidence in a professional and authoritative tone; the term originated from

First Day Review

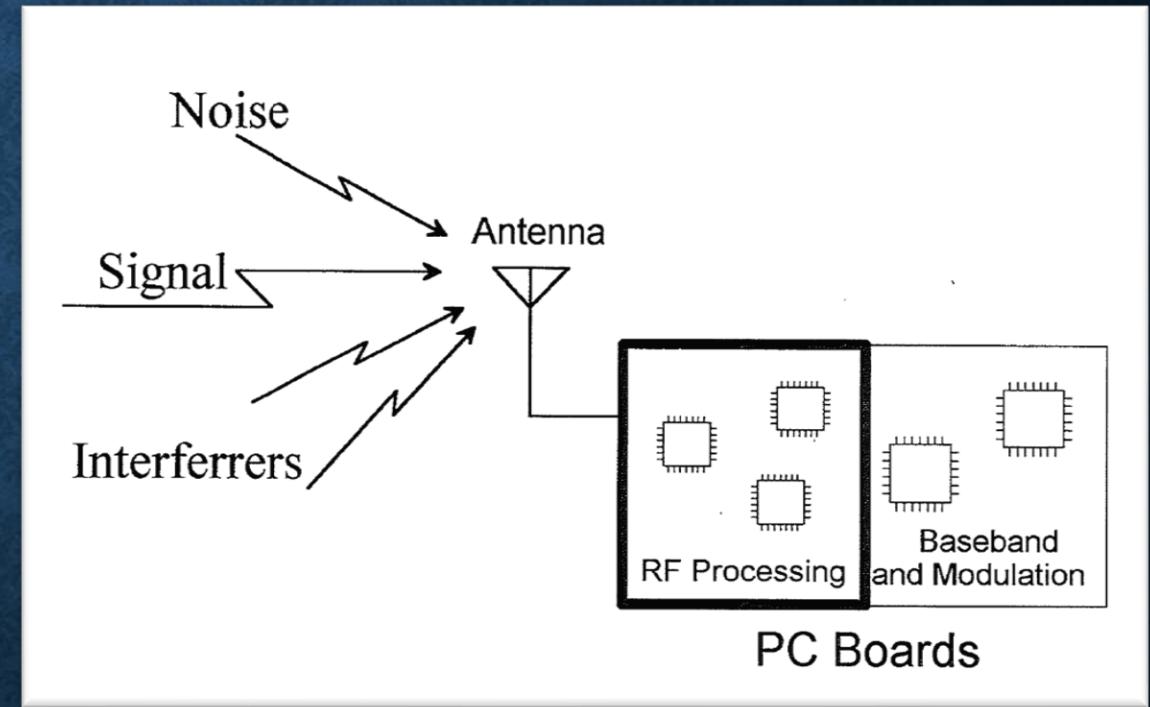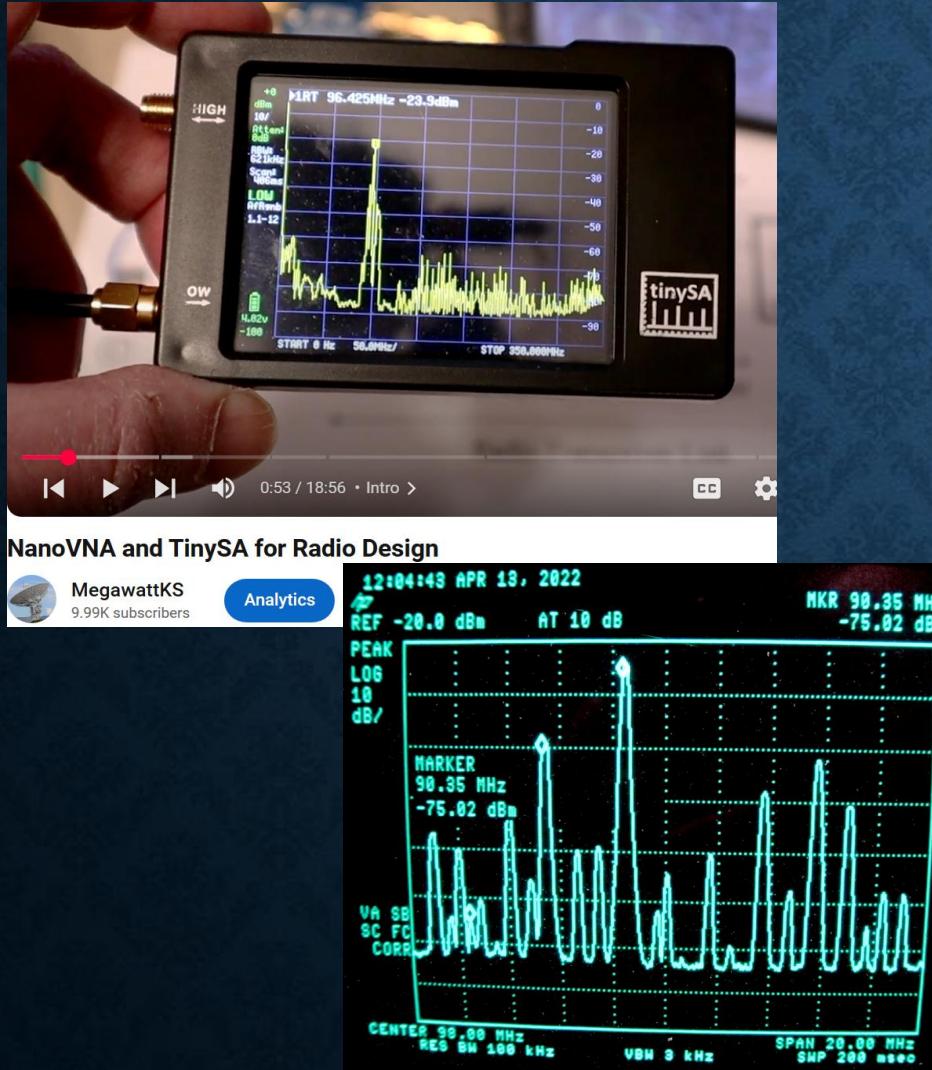

Radio Performance Testing


(From Radio Design 101 – Epilogue 1)

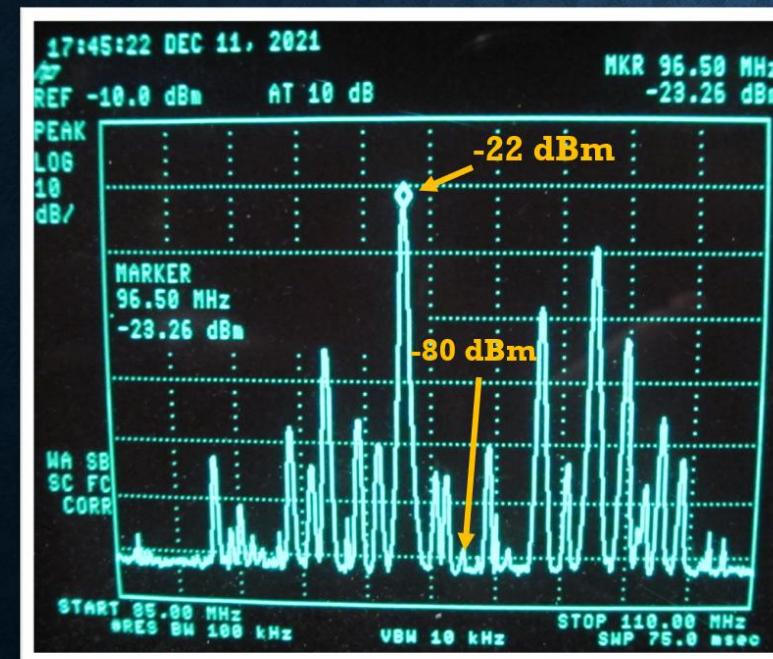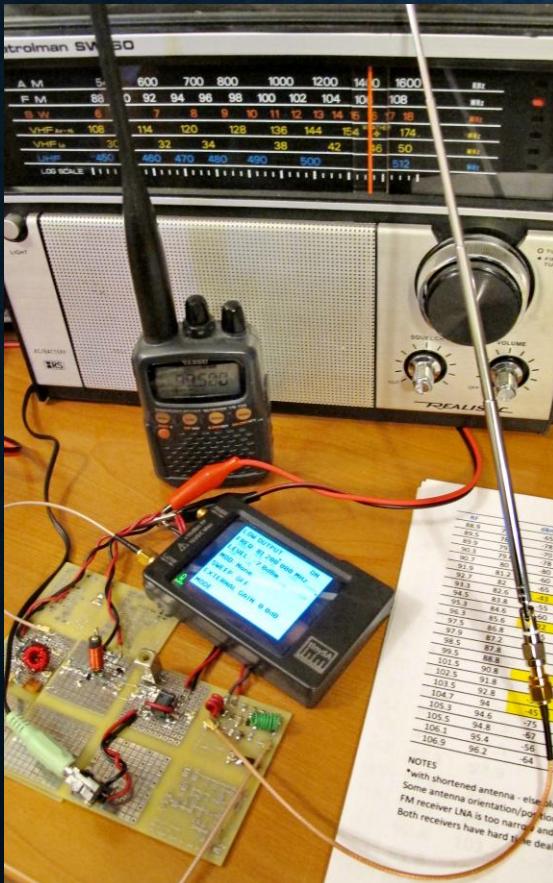

RF	LO	dBm	FMrx	FMrxFixed	VR120	VR120atten	Old Radio
88.9	78.2	-65					yes yes
89.5	78.8	-78					yes yes
89.9	79.2	-70	quiet	quiet	yes	yes	yes
90.3	79.6	-78			quiet		yes
90.7	80	-80					yes
91.9	81.2	-60	quiet	good	yes	yes	yes
92.7	82	-65		good			yes
93.3	82.6	-43	excellent	excellent	yes	yes	yes
94.5	83.8	-55	quiet	good	yes	yes	yes
95.3	84.6	-60	quiet	good	yes	yes	yes
96.3	85.6	-22	excellent	excellent	yes	yes	yes
97.5	86.8	-65		good			yes
97.9	87.2	-67	quiet	quiet	yes	yes	yes
98.5	87.8	-80					?
99.5	88.8	-61	?	excellent*			yes
101.5	90.8	-40	excellent	excellent	yes	yes	yes
102.5	91.8	-62					yes
103.5	92.8	-30	excellent	excellent	yes	yes	yes
104.7	94	-45	good	excellent	yes	yes	yes
105.3	94.6	-75					yes
105.5	94.8	-67					yes
106.1	95.4	-56	very quiet	yes	yes	yes	yes
106.9	96.2	-64					yes


Today's Topic – The Intermod Problem

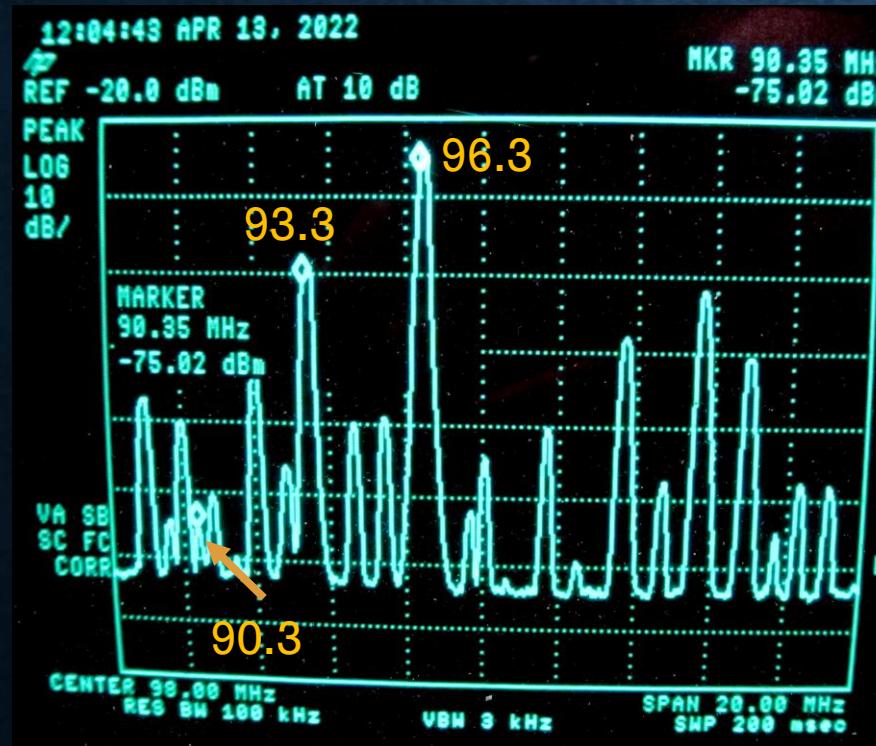Two strong signals at 96.3 and 93.3 MHz ‘mix’ and block weaker (-75 dBm) signal at 90.3 MHz



Result – Using New Technology

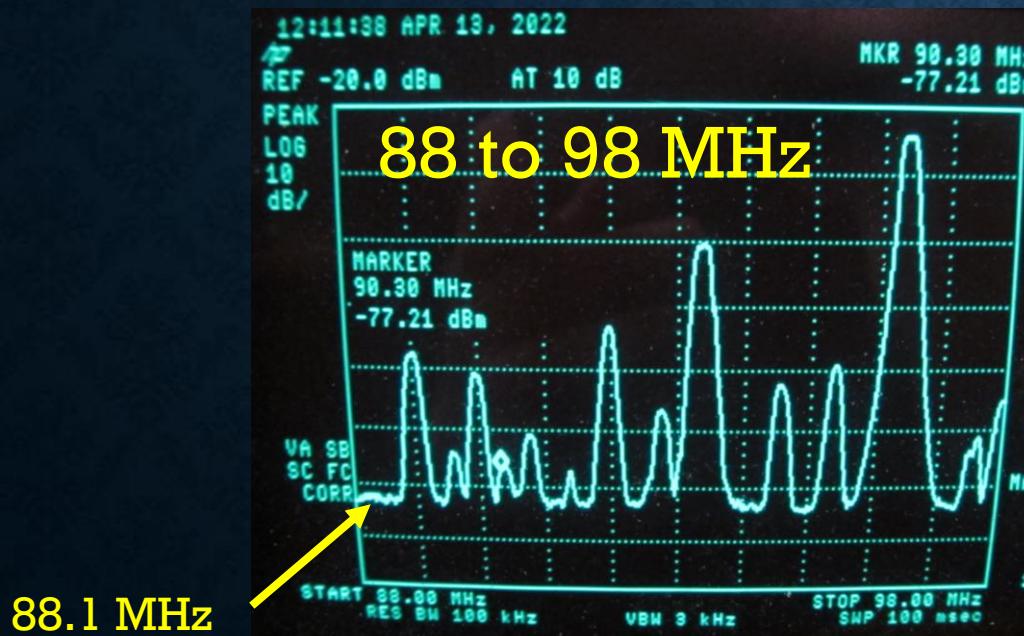*RD101 Radio Out-performed all 3 Commercial Ones !
(when using 200 kHz bandwidth Q-enhanced Front-End filter)*





Station	dBm	ATS 25	VR-120	SW-60	RD-101*
88.1	-96				
88.9	-58				
89.5	-75				
89.9	-61				
90.3	-77				
90.5	-85				
90.7	-71				
91.3	-80				
91.9	-55				
92.5	-82				
92.7	-70				
93.3	-41				
94.5	-63				
95.3	-60				
96.3					
97.5					
97.9					

A yellow arrow points to the RD-101* column header, with the text "With Q-enhanced filter front-end added" positioned next to it.


Below the table are three small images: a handheld radio, a benchtop radio receiver, and a close-up of a circuit board labeled "Q ENHANCED FILTER CORE".

New Q-Enhanced LNA


From Radio Design 101 – Epilogue 3

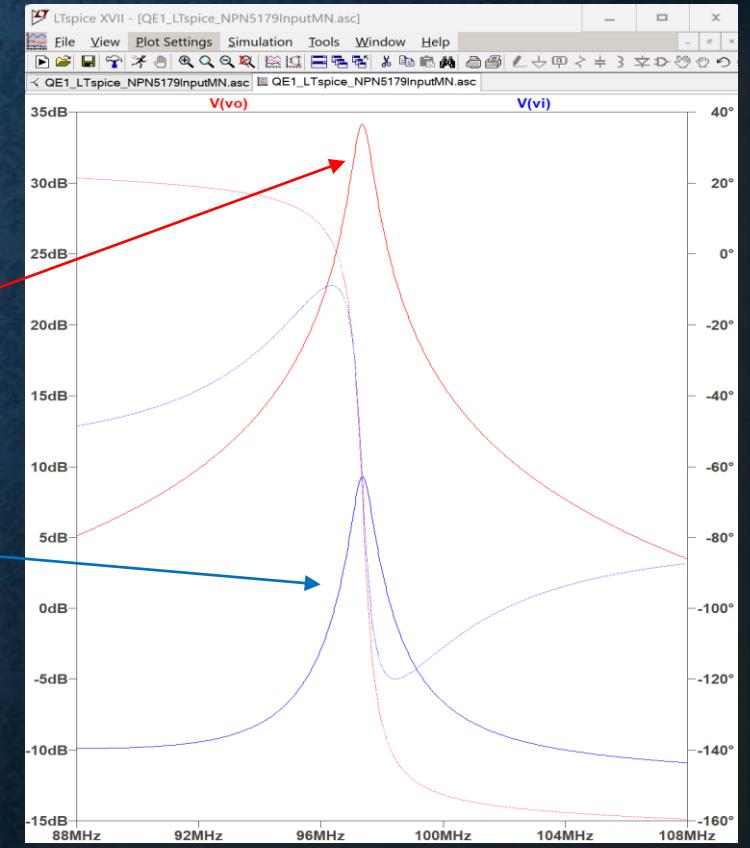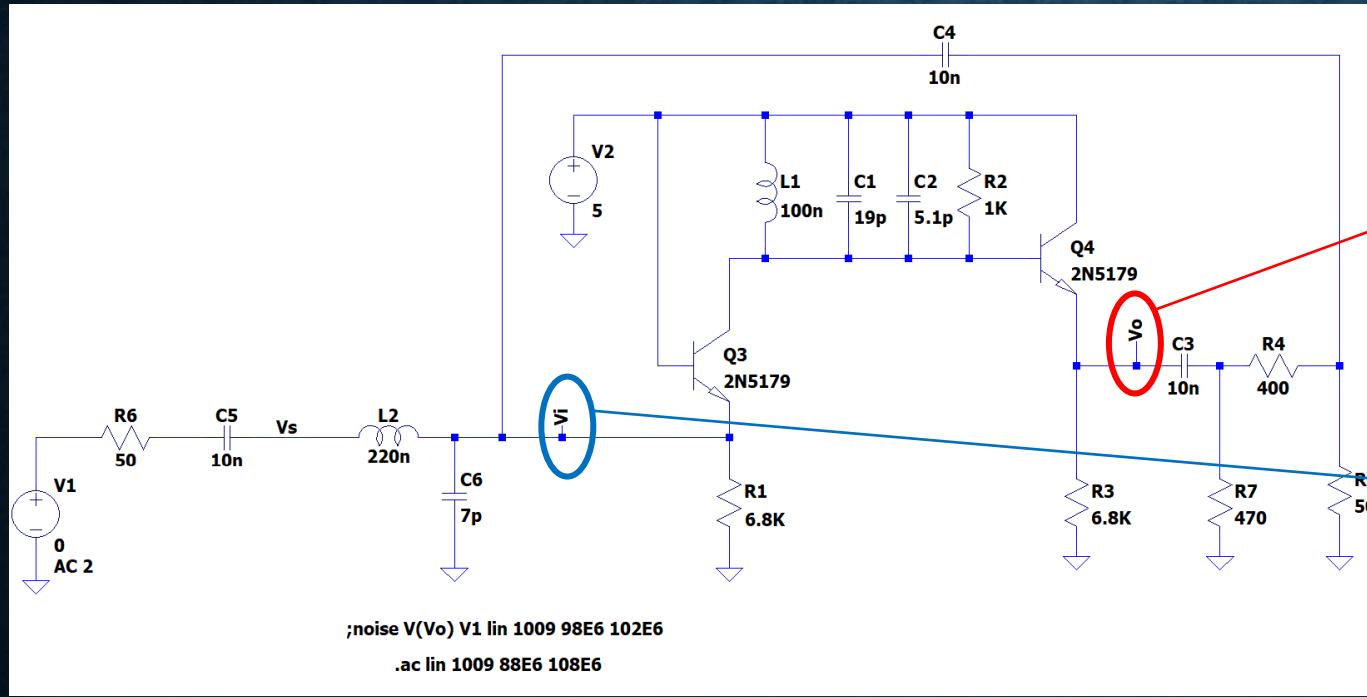

Intermod and Noise Figure Sims


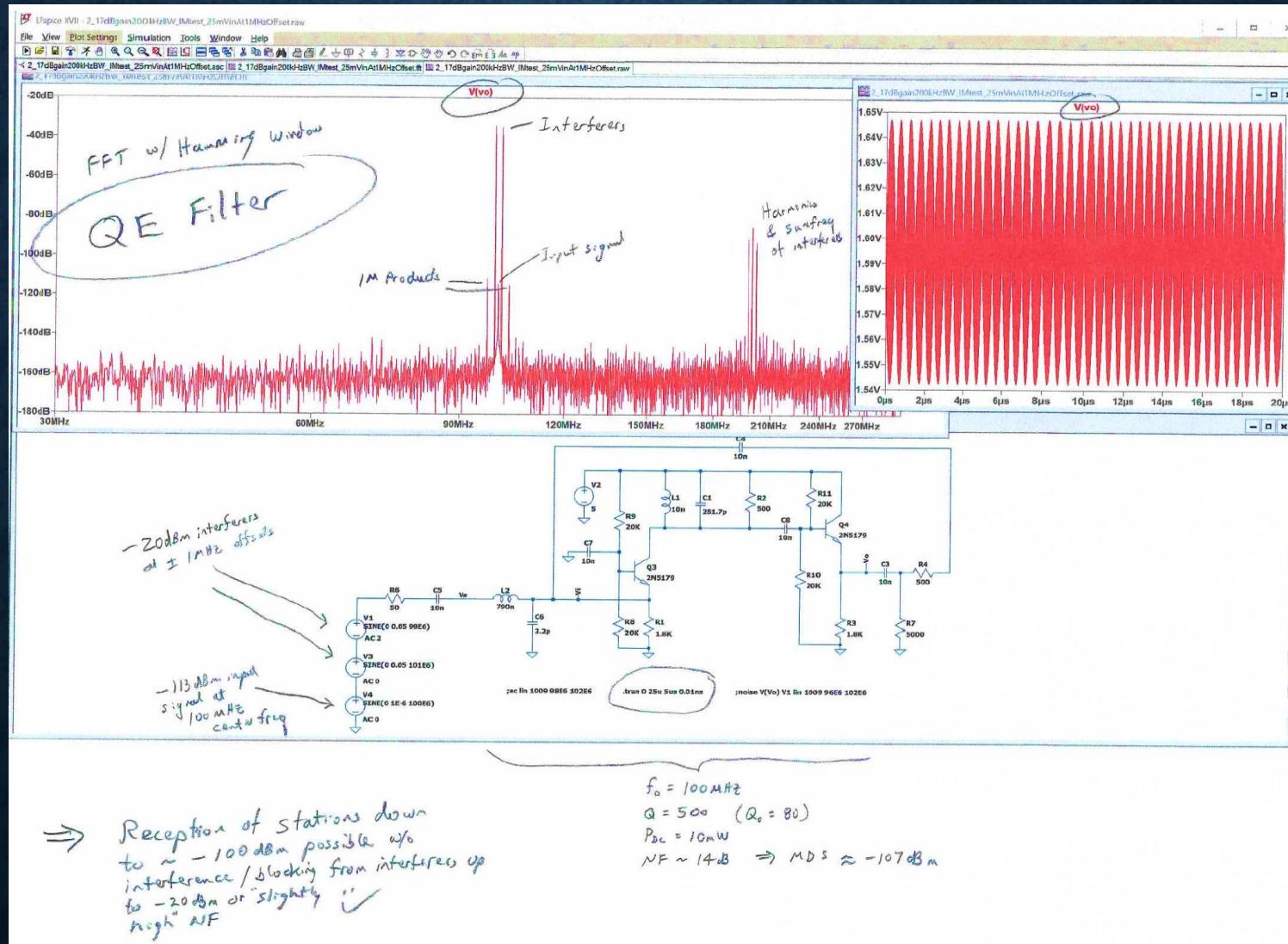


vs Traditional Low-Power LNA

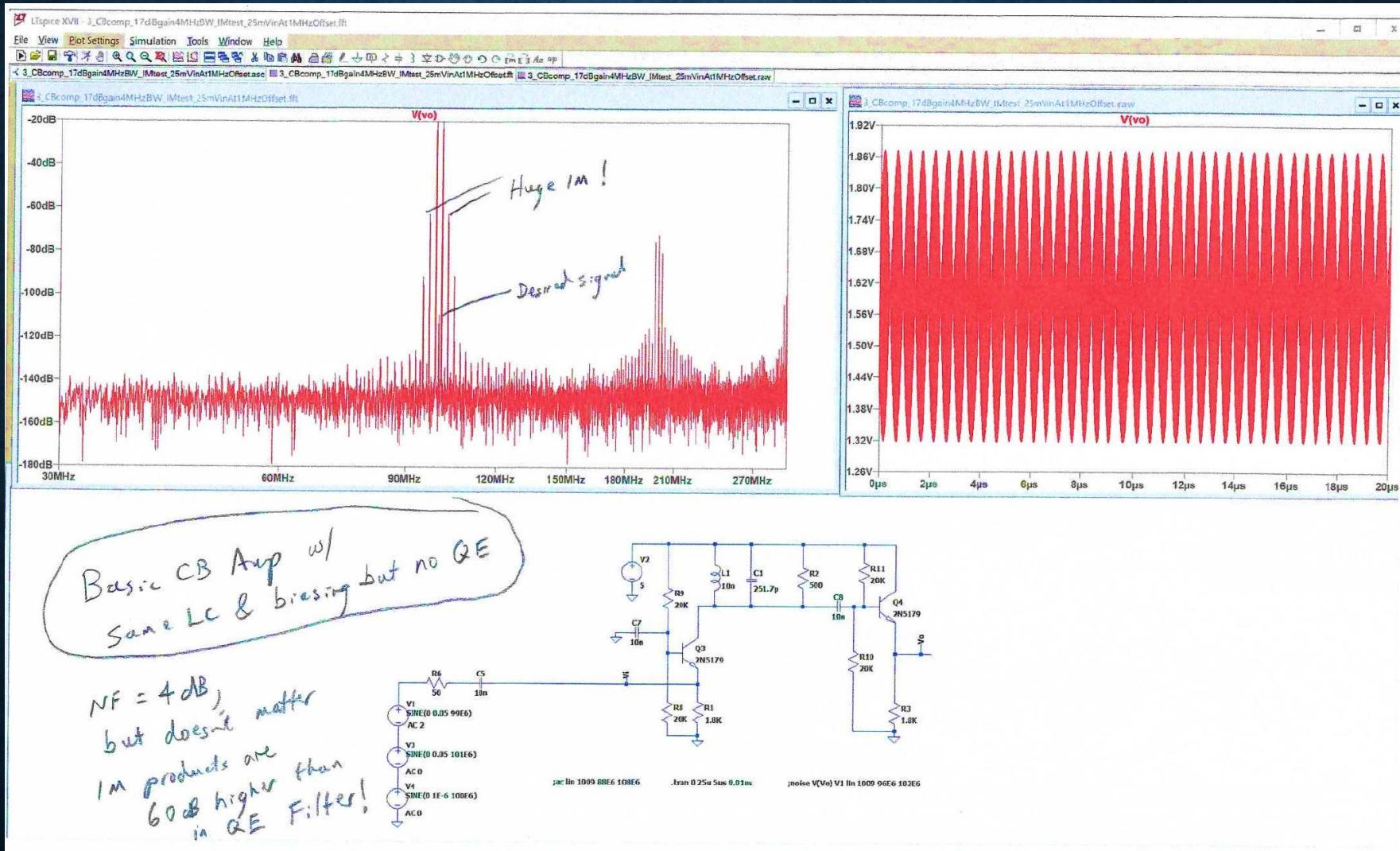

Radio Design 401

Episode 1 *Part 2*

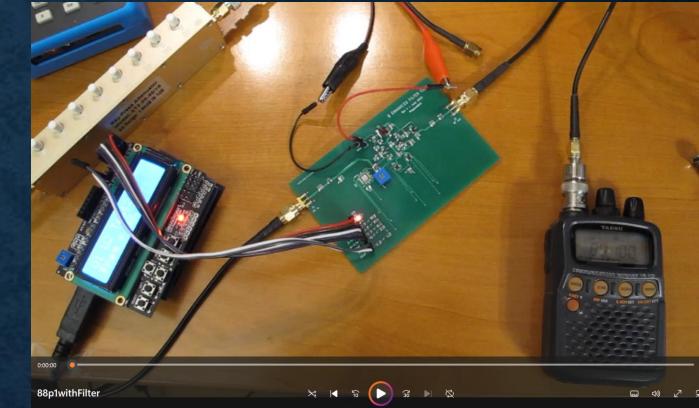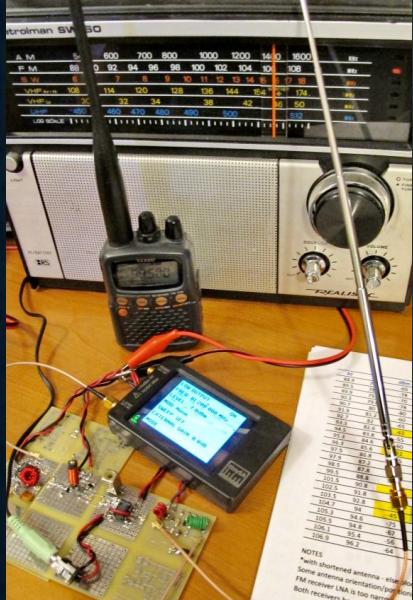


*Low-power Receivers in
Crowded Spectrum Environments*

Today's Outline

- • *Intermodulation Problems and Solutions*
- *Basic Research in Low Power Receivers*
- *Circuit-level Solution Examples*
- *Future Episodes in This Series*

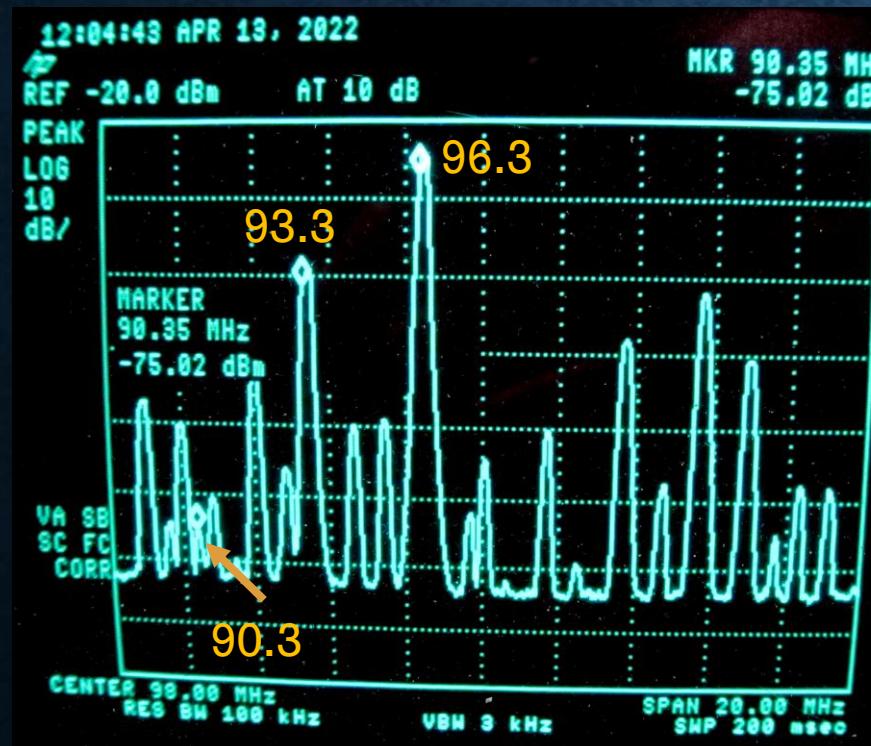Part 1 Review – The Intermod Problem

Two strong signals at 96.3 and 93.3 MHz ‘mix’ and block weaker (-75 dBm) signal at 90.3 MHz



Receiver Architectures - Radio Design 101 Final Epilogue **Timestamp 7:43**



MegawattKS
9.87K subscribers

Analytics


Edit video

148

Share


Promote

Problem Origins

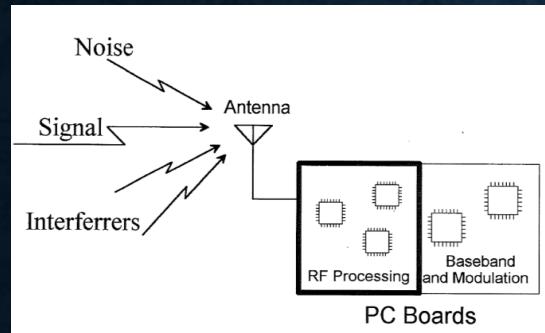

Strong signals inside preselect filter passband can overwhelm weak ones !

Blocking Problem

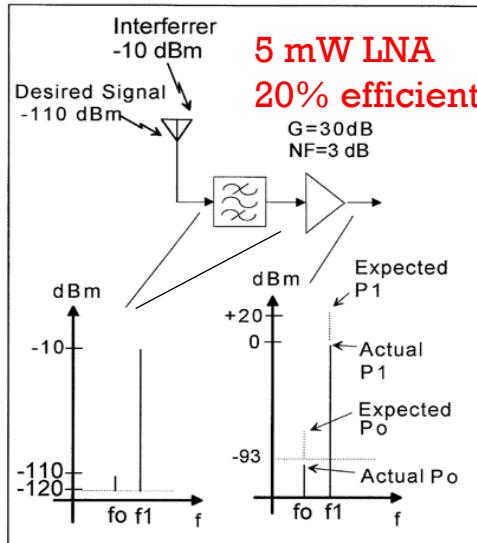

Effects

Gain compression
Desired signal below noise floor at output


Solutions

Use higher power LNA
Decrease LNA gain
Filter out f_1

NOTE

Could occur in later stages also **Like Mixer !!**

Intermod Problem

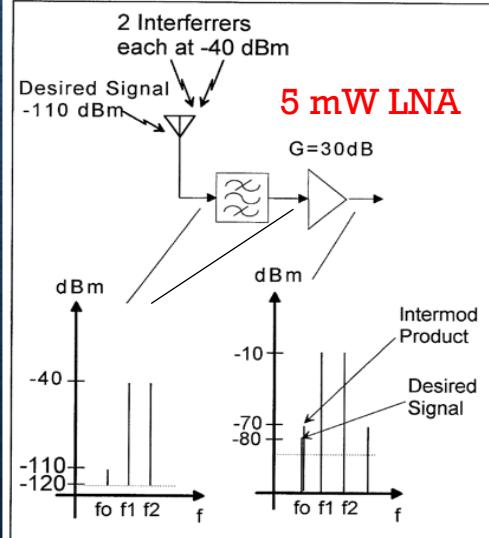

Effects

LNA generates "intermod products" at $2f_2-f_1$ & $2f_1-f_2$.
Product at $2f_1-f_2 = f_0$ overpowers desired signal.



Solutions

Use higher power LNA.
Decrease LNA gain.
Filter out f_1, f_2



NOTE

Could occur in later stages also (especially mixer.)

Non-linear Distortion & Compression

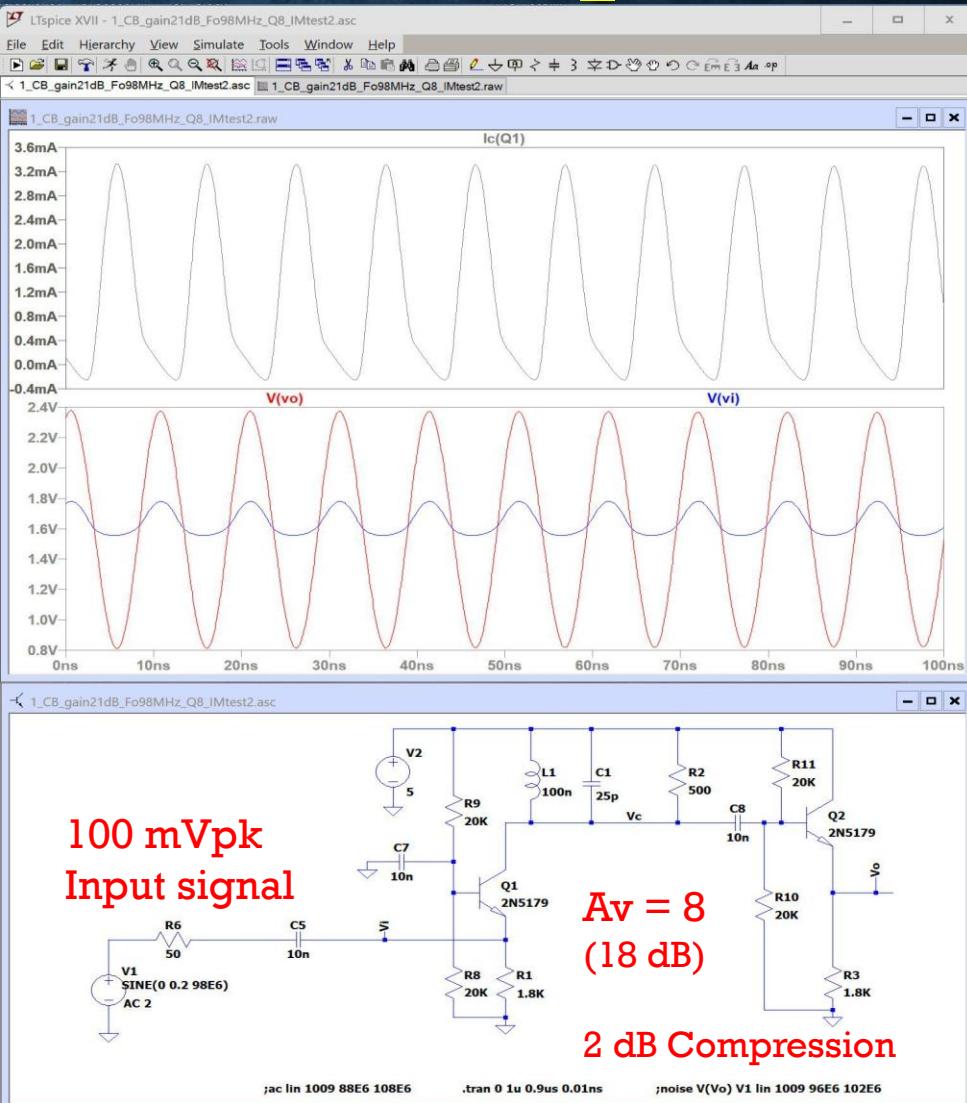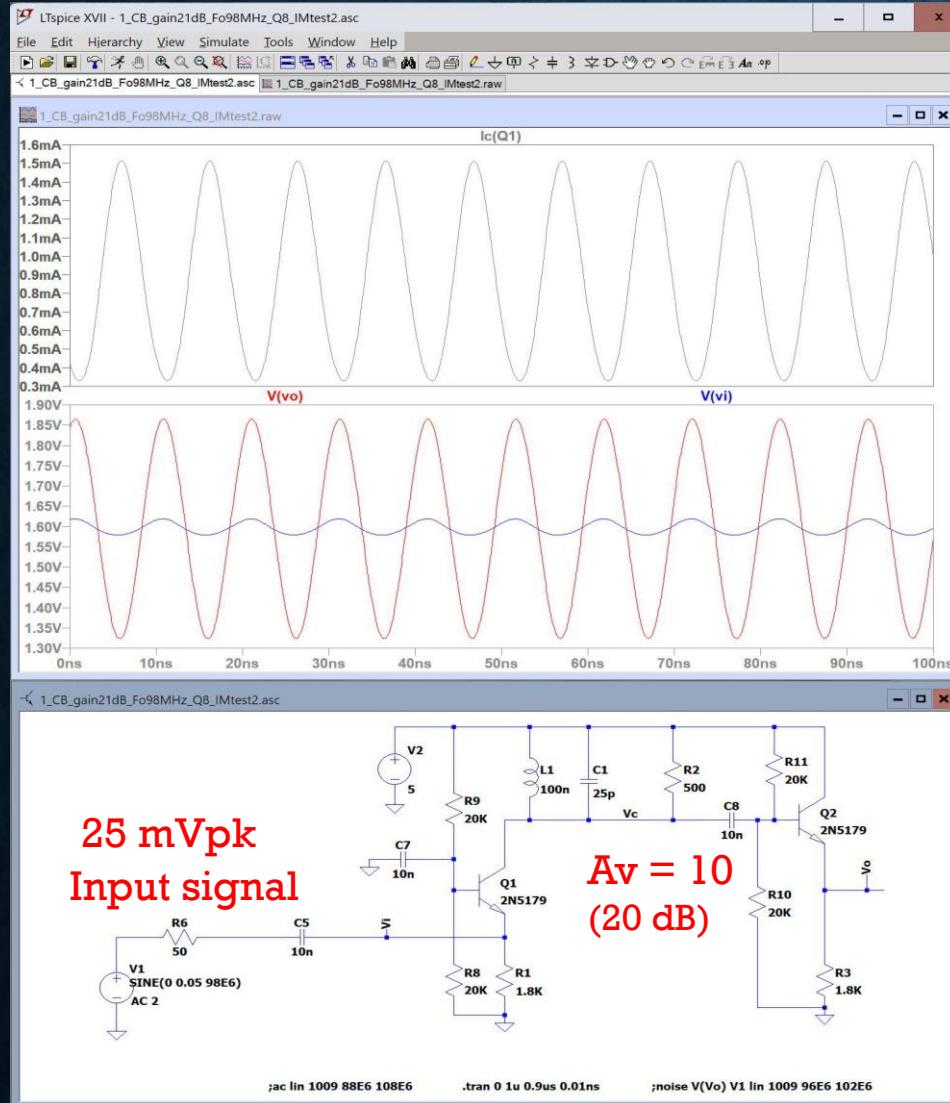


Intermod Simulation

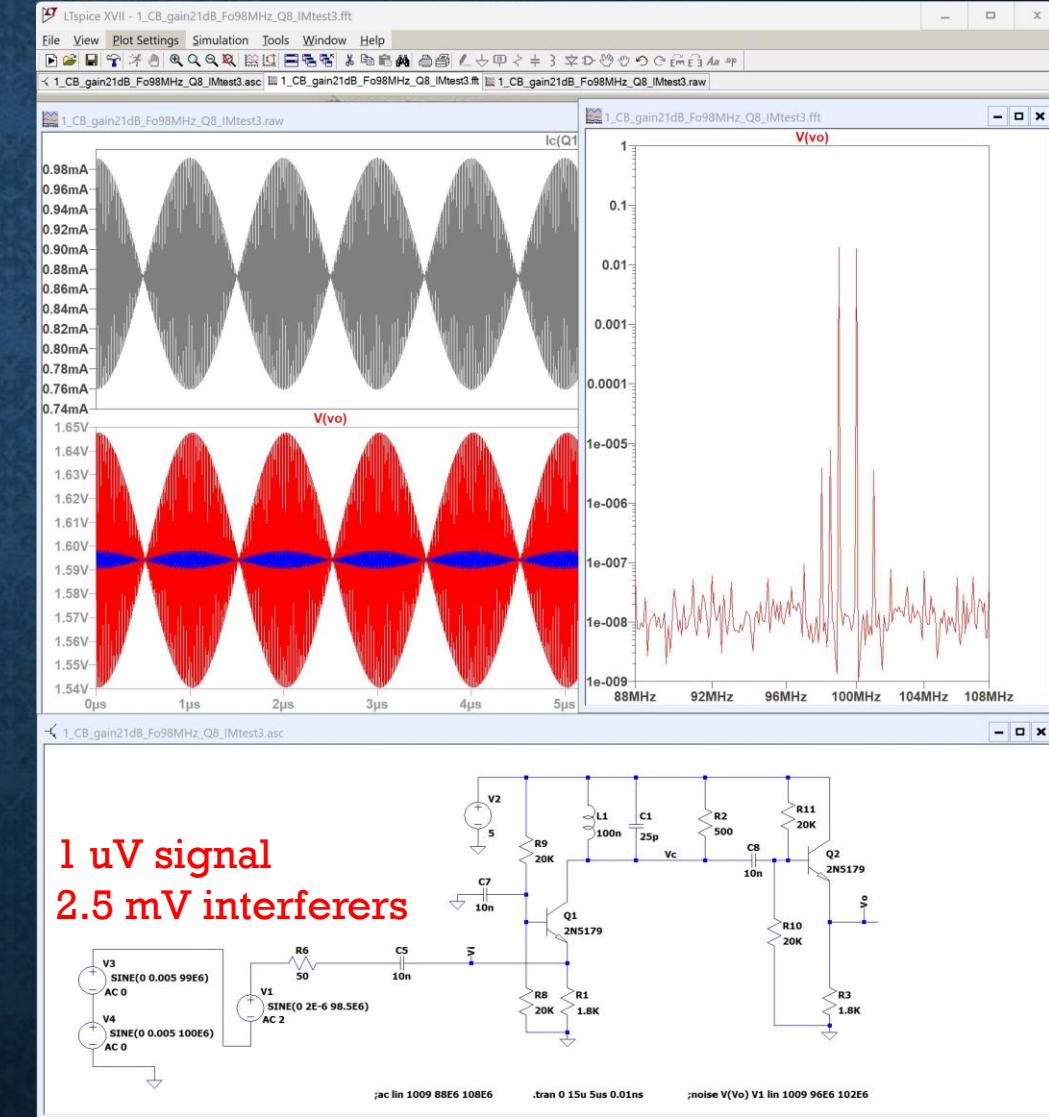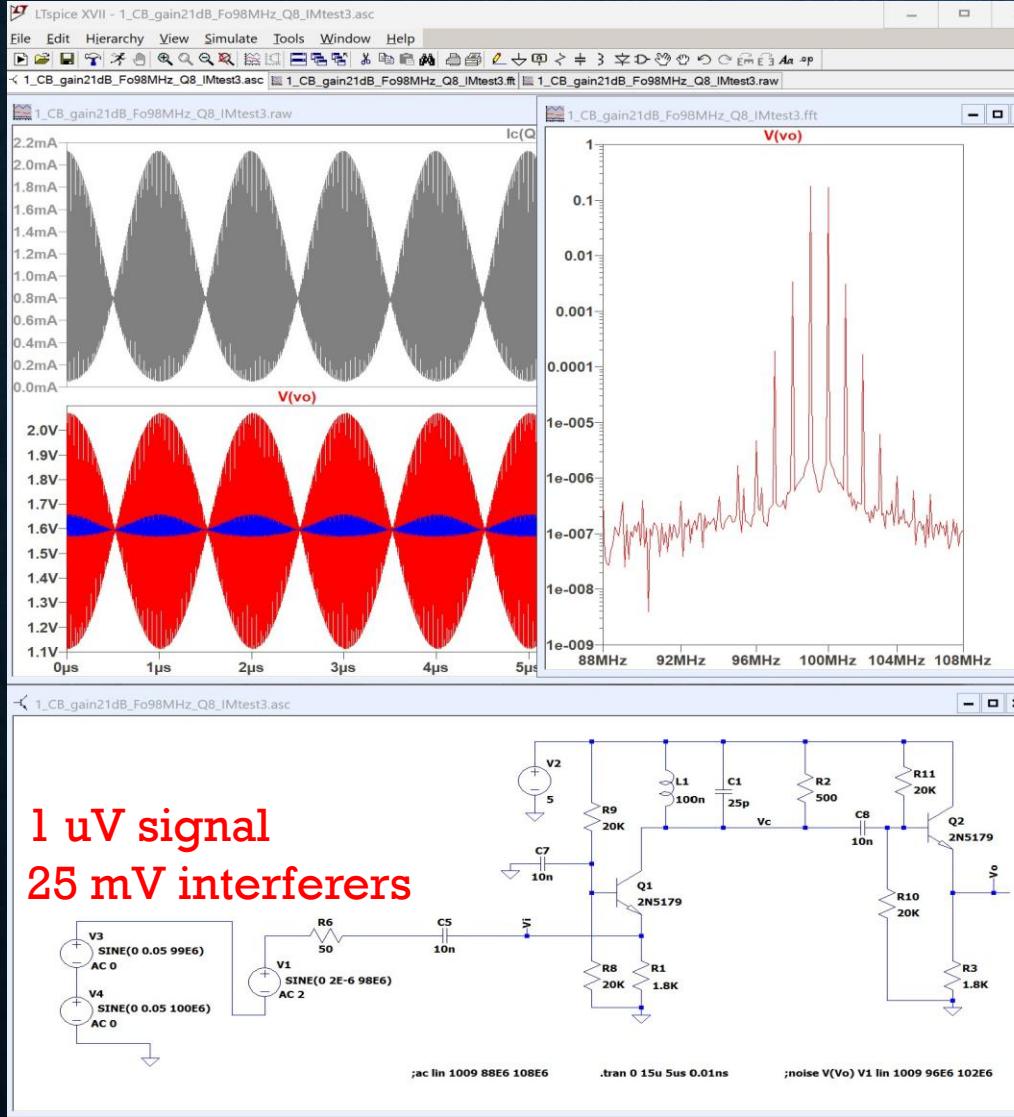

Proposed Solution

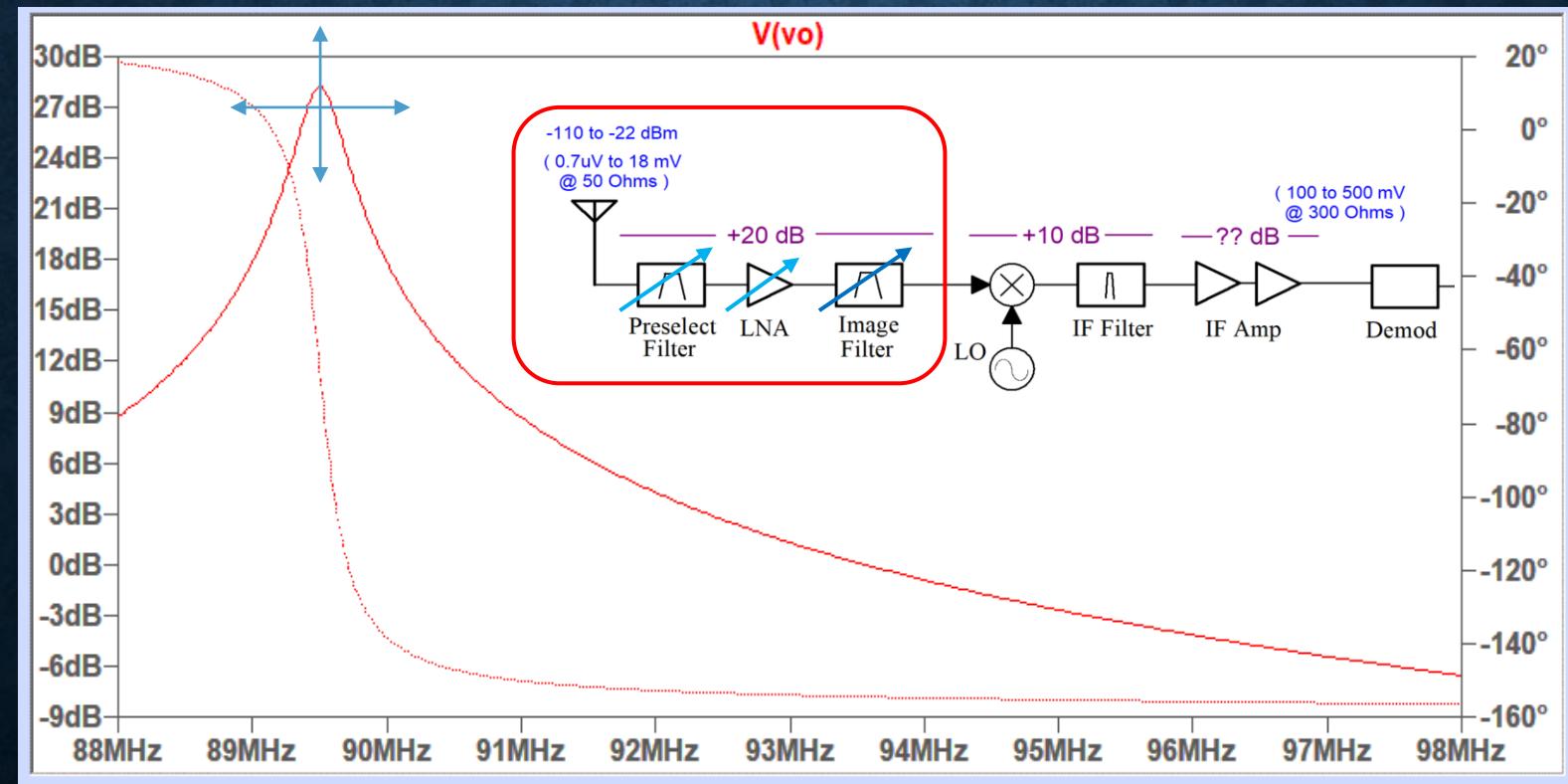
*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Q-enhanced Filter 1st Prototype




(From Radio Design 101 Epilogue 3)

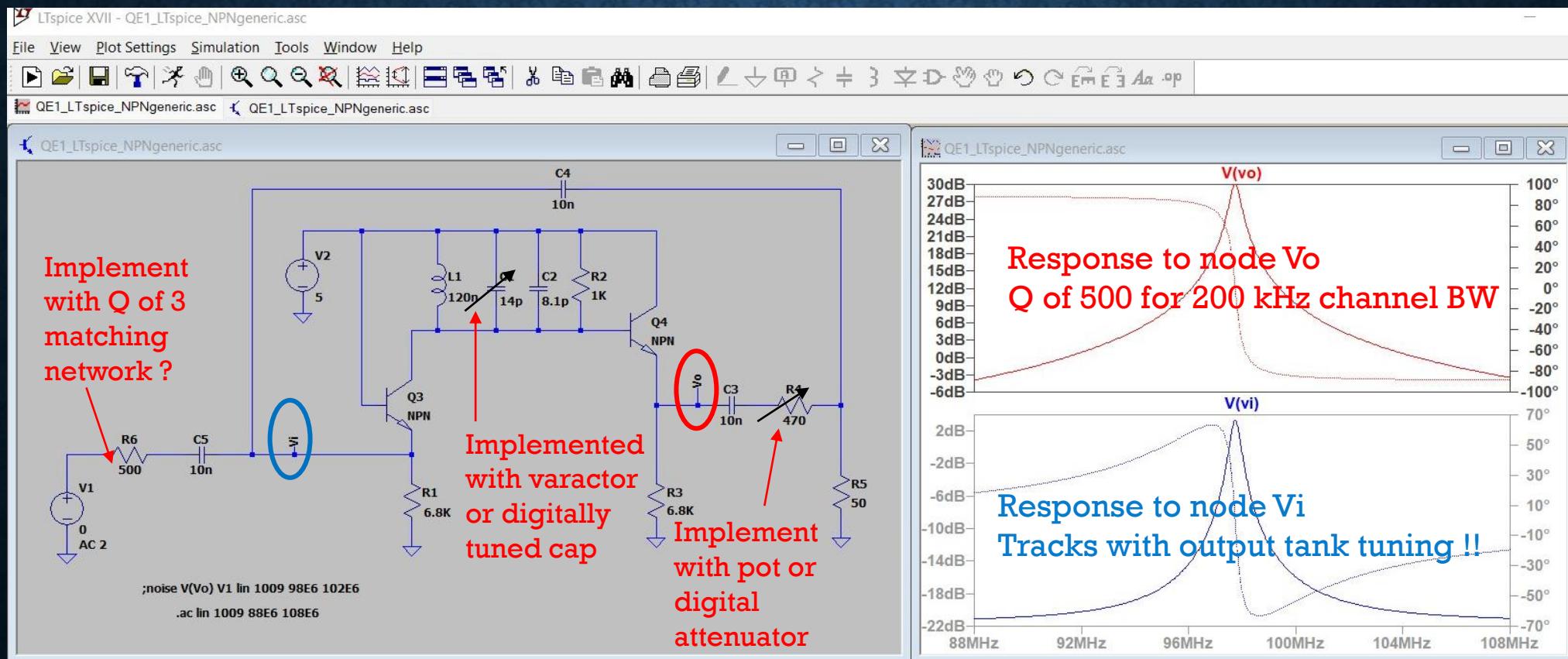Important: Provides filtering before Q3 !





1.2 mA at 5 V (6 mW)


25+ dB Improvement in SIR

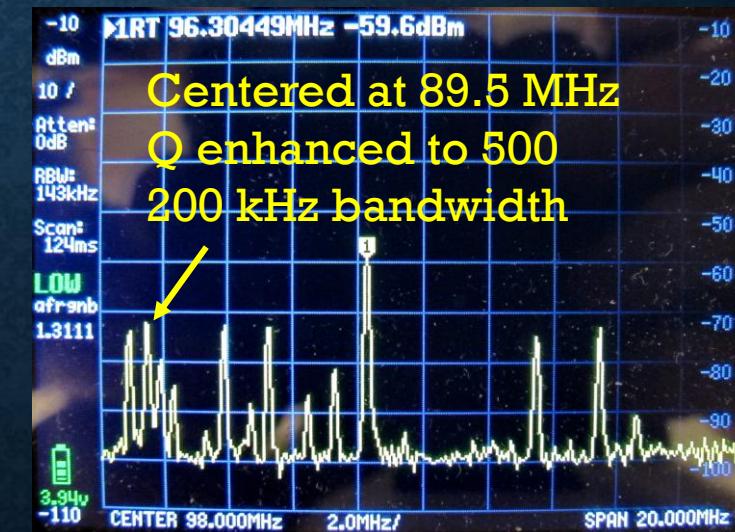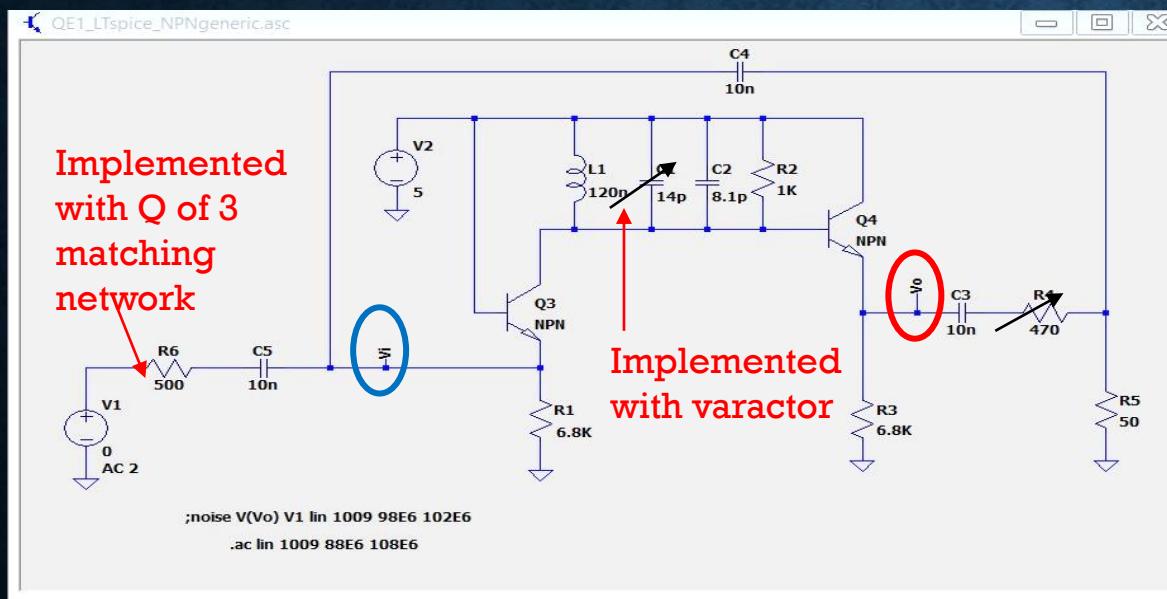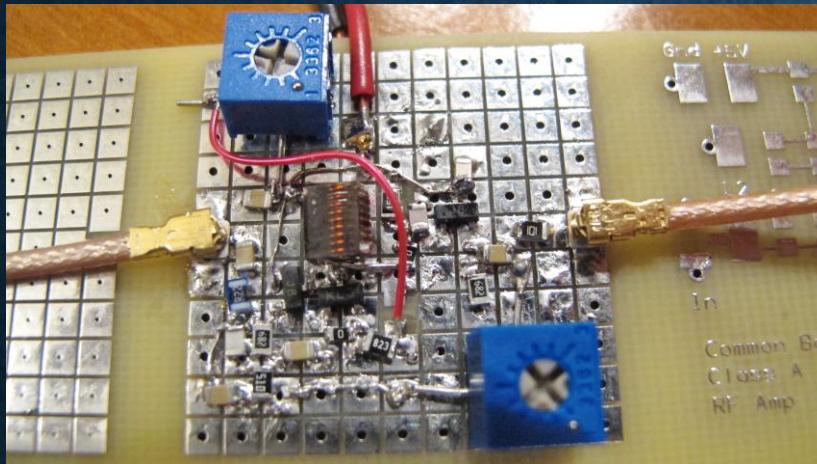

Pulling out Really Weak Signals !

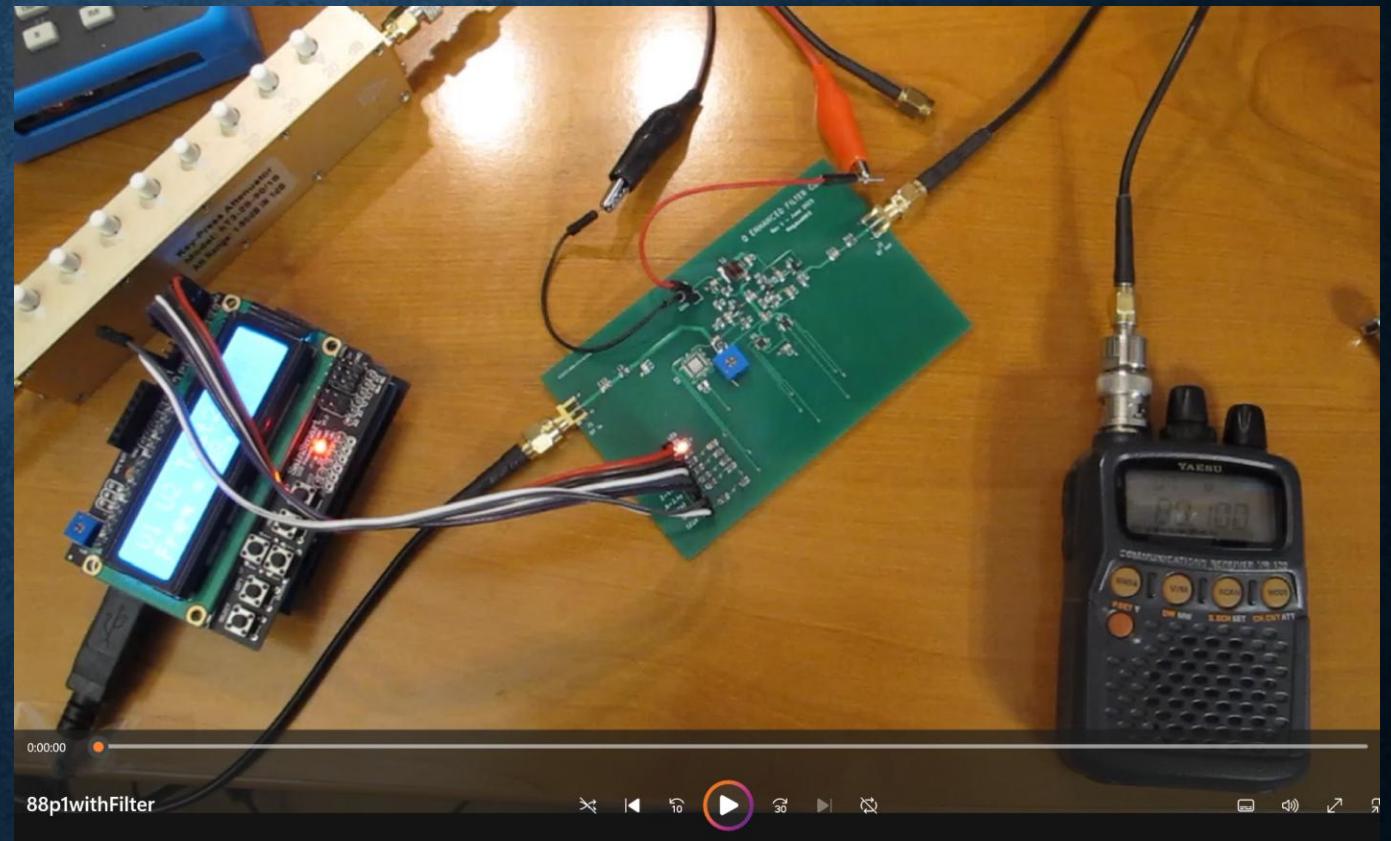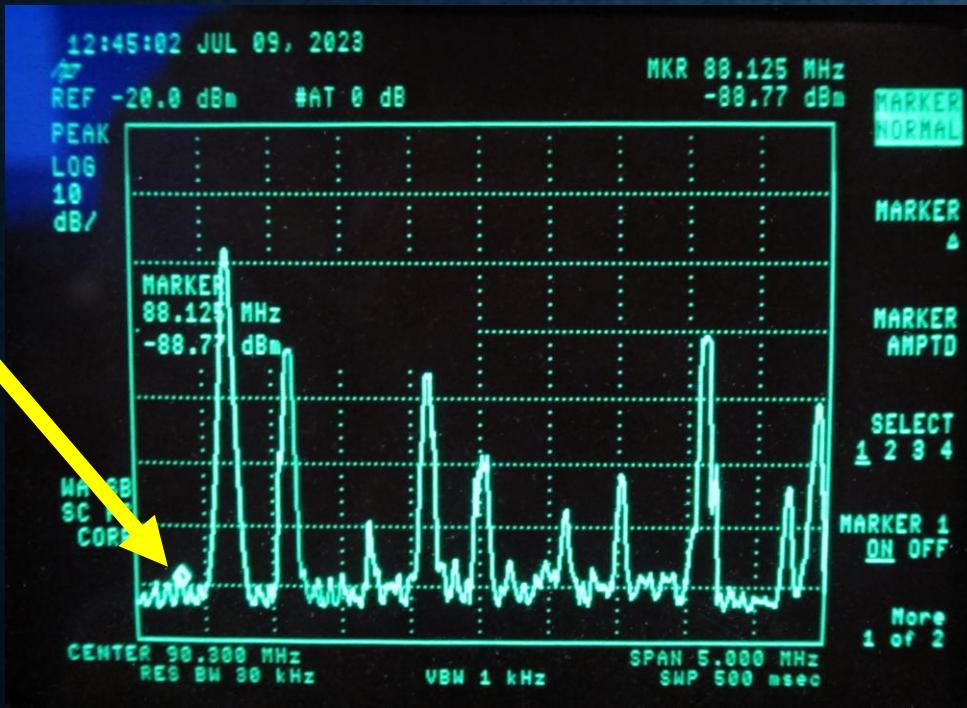

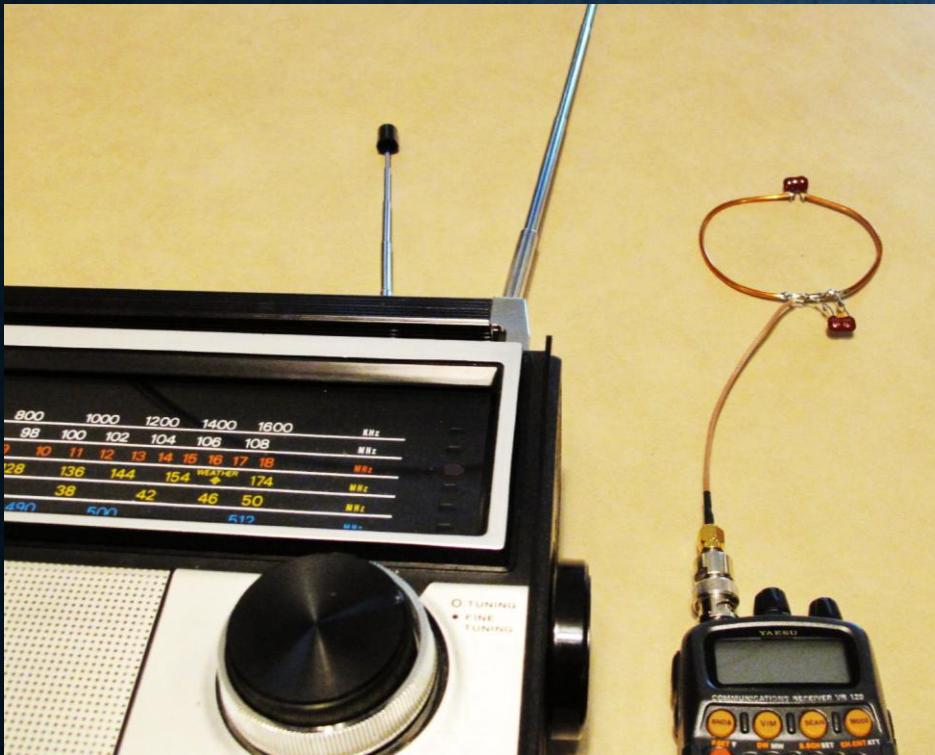Additional Solutions Directional and/or High Q Antennas



Q-Enhancement and Digitally Tuned Caps

Antenna integrated with Q-enhanced LNA

pSemi
Product Specification
PE64102
UltraCMOS® Digitally Tunable Capacitor (DTC) 190–3600 MHz

General Description
The PE64102 is a DuBiETM-enhanced digitally tunable capacitor (DTC) device. It is based on pSemi's UltraCMOS® technology. DTC products provide a monolithic integrated impedance tuning solution for demanding RF applications. They offer excellent performance change versus bias state and excellent harmonic performance compared to varactor-based tunable solutions.

Features

- 8-bit (SPI compatible) 8-bit serial interface with built-in bias voltage generation and reverse-by mode for reduced power consumption
- DuBiETM-enhanced UltraCMOS® device

Figure 1. Functional Block Diagram

Small Loop Antennas for FM / VHF / UHF Radio Receivers - Antenna Briefs #9

MegawattKS
9.88K subscribers

Analytics Edit video

237 Share ...

Today's Outline



- ✓ • *Introduction*
- • ***Basic Research in Low Power Receivers***
 - *Circuit-level Solution Examples*
 - *Future Episodes in This Series*

Please cite as <https://www.youtube.com/user/MegawattKS>

Some Radios Through the Years

(See Part 1 & Radio Design 101, Epilogue 3)

1970s and 1980's HF radios

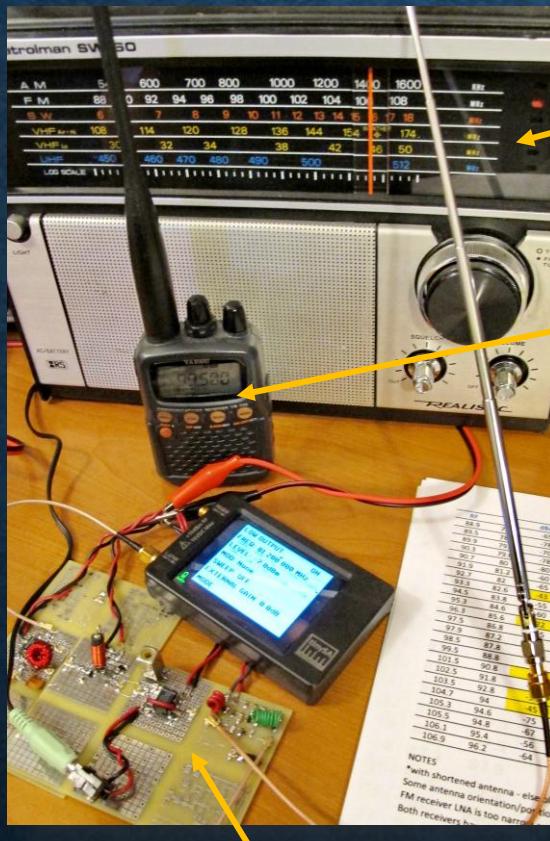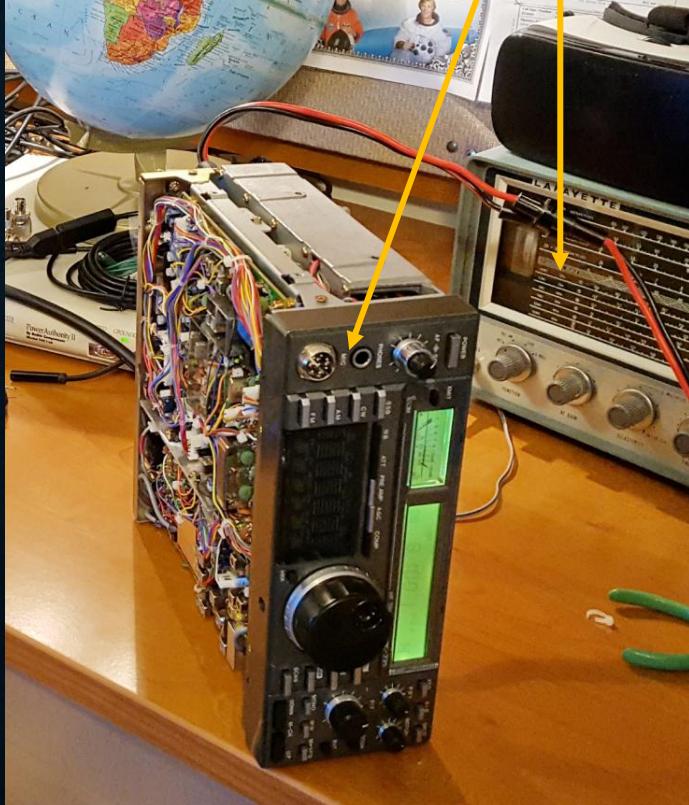

1990 Portable multi-band receiver
(Patrolman SW-60)

2022 Homebrew FM superhet
(From Radio Design 101 series)

2003 Yaesu wideband handheld receiver
(VR-120)



2024 Software-Defined
Radio (ATS-25)


Origins of This Research

4 Alternative Receiver Architectures	93
4.1 Early Receiver Architectures	94
4.1.1 Tuned RF Receivers	94
4.1.2 Regenerative Receivers	96
4.1.3 Super-Regenerative Receivers	98
4.2 Superheterodyne Receivers	100
4.2.1 Modern Single Conversion Implementations	101
4.2.2 Multiple Conversion Implementations	102
4.2.3 Up Conversion Implementations	104
4.2.4 Designs with Ultra-Low IFs	106
4.2.5 Designs with Image Rejection Mixers	108
4.2.6 Designs with Selective Demodulators	109
4.3 Direct Conversion Receivers	110
4.4 Digital Receivers	113
4.5 Ideal Low-Power Receivers	115

From: “[Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies](#)”,
William B. Kuhn, PhD dissertation, Virginia Tech, 1995 .

Some Related Research Papers

The screenshot shows a search result for a paper on IEEE Xplore. The title is "Dynamic range performance of on-chip RF bandpass filters". It is published by IEEE. The abstract discusses the challenges of implementing RF bandpass filters on-chip due to performance requirements. The paper has 61 cites in papers and 1424 full text views. The URL is <https://ieeexplore.ieee.org/abstract/document/1237356>.

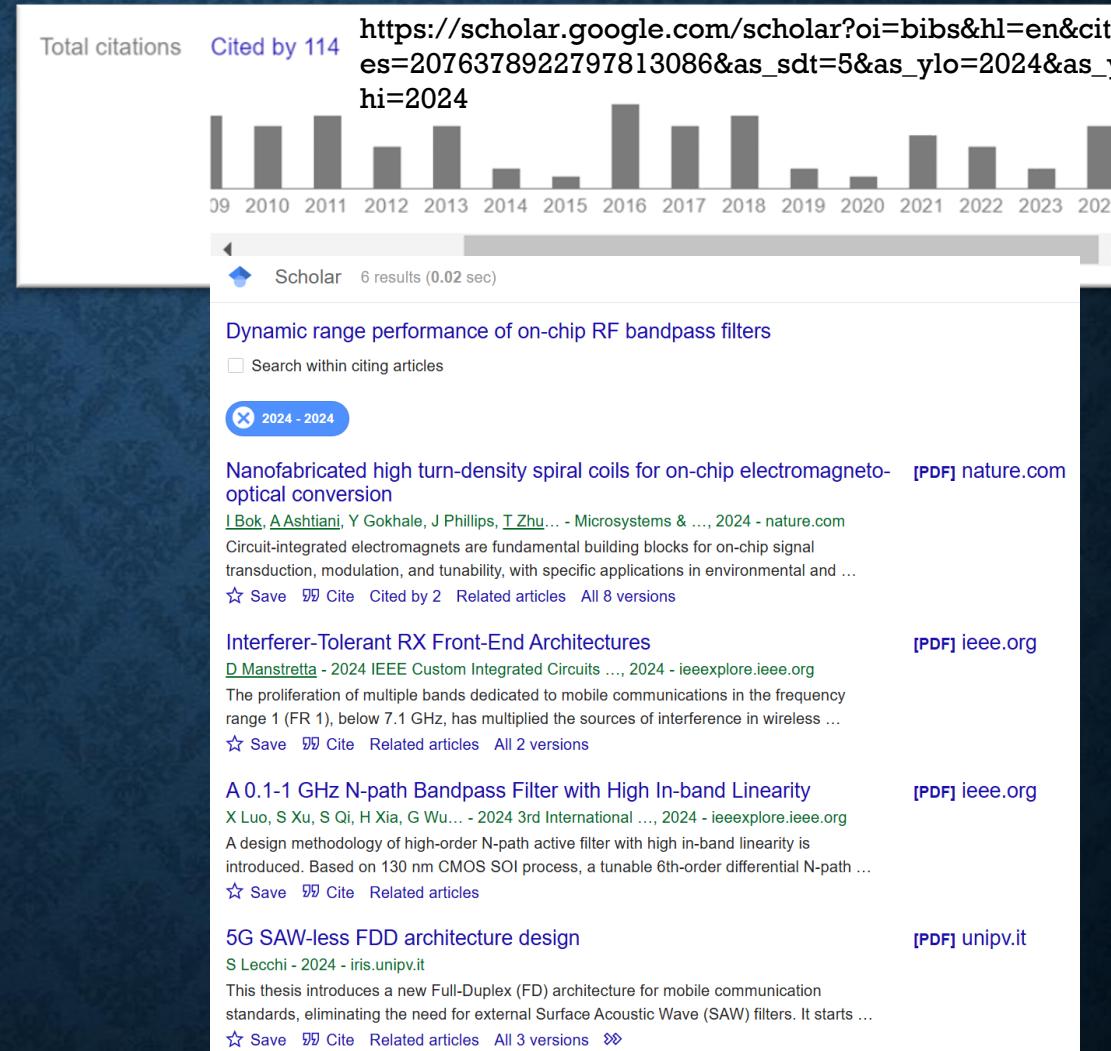

Why Does this Research Matter ?

- Receive more stations !
- Also ...
 - Spectrums have become more crowded
 - Need more efficient use of spectrum resources
 - Regulatory agencies are focusing increasingly on receiver performance
 - ITU Internationally
 - NTIA and FCC in United States
 - Low-power consumption is good for IOT and energy harvesting radios
 - Power reductions of 10x to 100x or more may be possible

Regulatory Focus on Receivers

2023

FCC FACT SHEET*

Principles for Promoting Efficient Use of Spectrum and Opportunities for New Services Policy Statement, ET Docket No. 23-122


Background: The demand for spectrum continues to grow dramatically. As the Commission continuously evaluates opportunities to identify new sources of licensed, unlicensed, and shared spectrum to satisfy this growing demand, it must find ways to promote more intensive use of spectrum while ensuring coexistence among both new and existing services.

This Policy Statement takes a fresh look at the Commission's spectrum management principles and provides guidance on how the Commission intends to manage spectrum efficiently and effectively going forward. In particular, it seeks to promote a balanced and comprehensive approach to spectrum management that holistically considers both the transmitter and receiver components of wireless systems, consistent with the goals of the FCC's April 2022 *Notice of Inquiry on Promoting Efficient Use of Spectrum through Improved Receiver Interference Immunity Performance* (ET Docket No. 22-173). The


<https://docs.fcc.gov/public/attachments/DOC-392197A1.pdf>

See also: <https://its.ntia.gov/publications/download/TR-03-404.pdf>

Radio Design 401



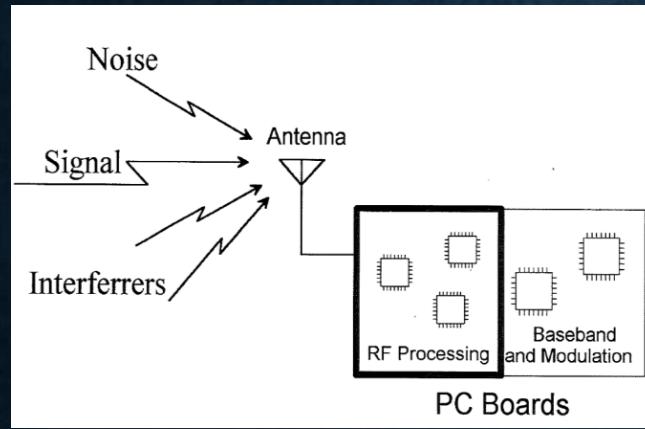


*Episode 1
Part 3 of 3*

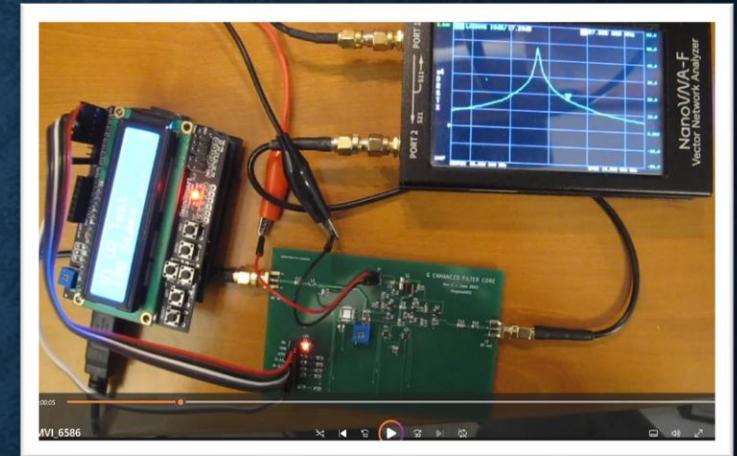


*Low-power Receivers in
Crowded Spectrum Environments*

Receiver Signal Environment

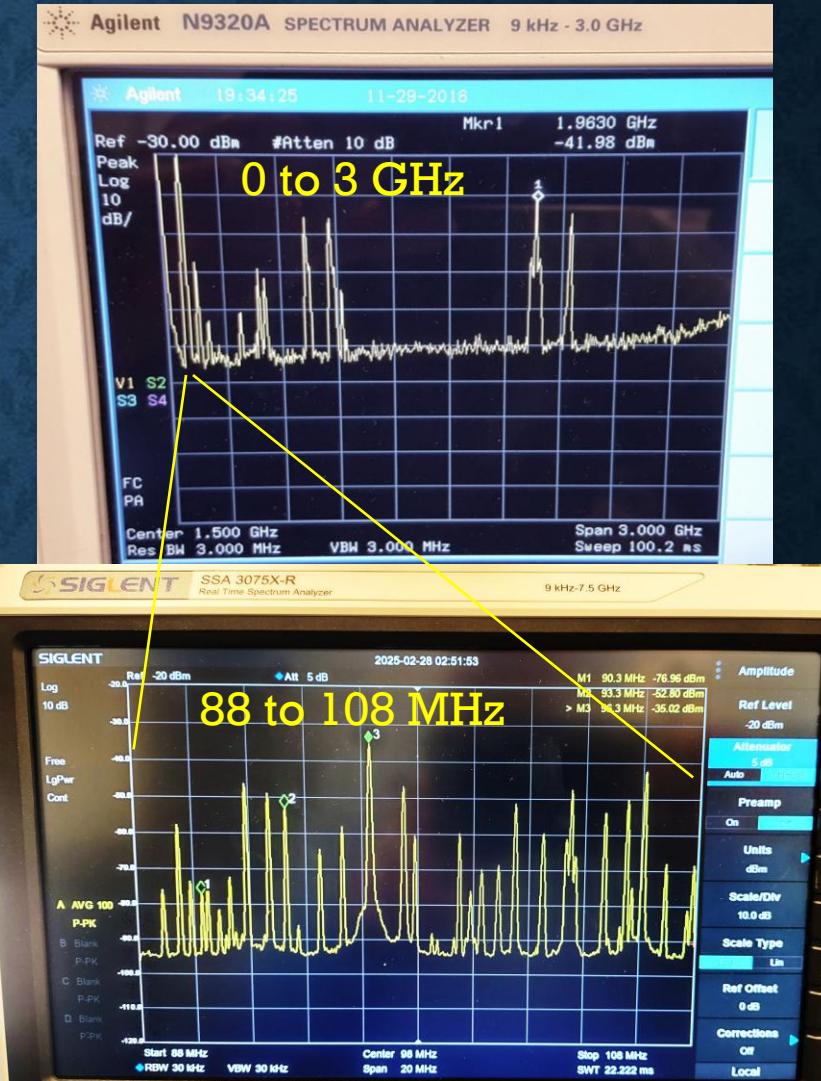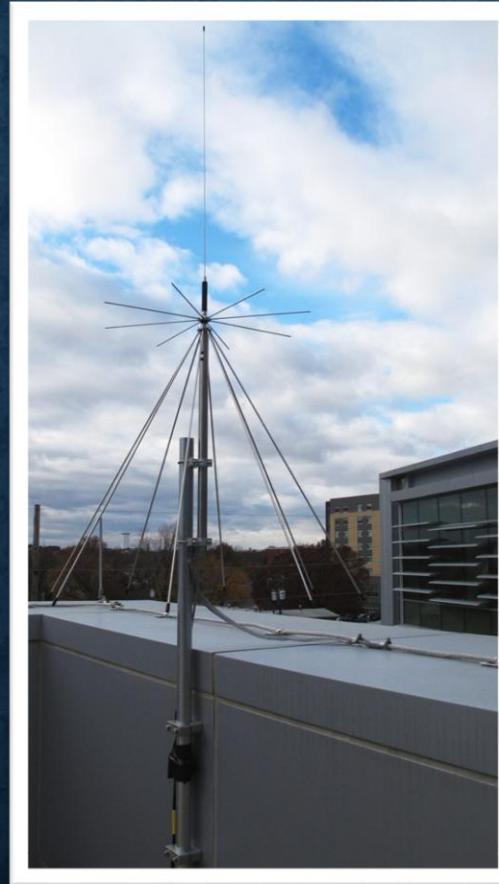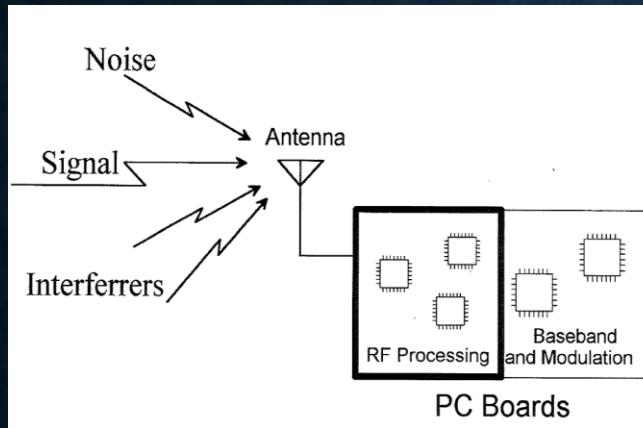


Classic Superhet Receiver

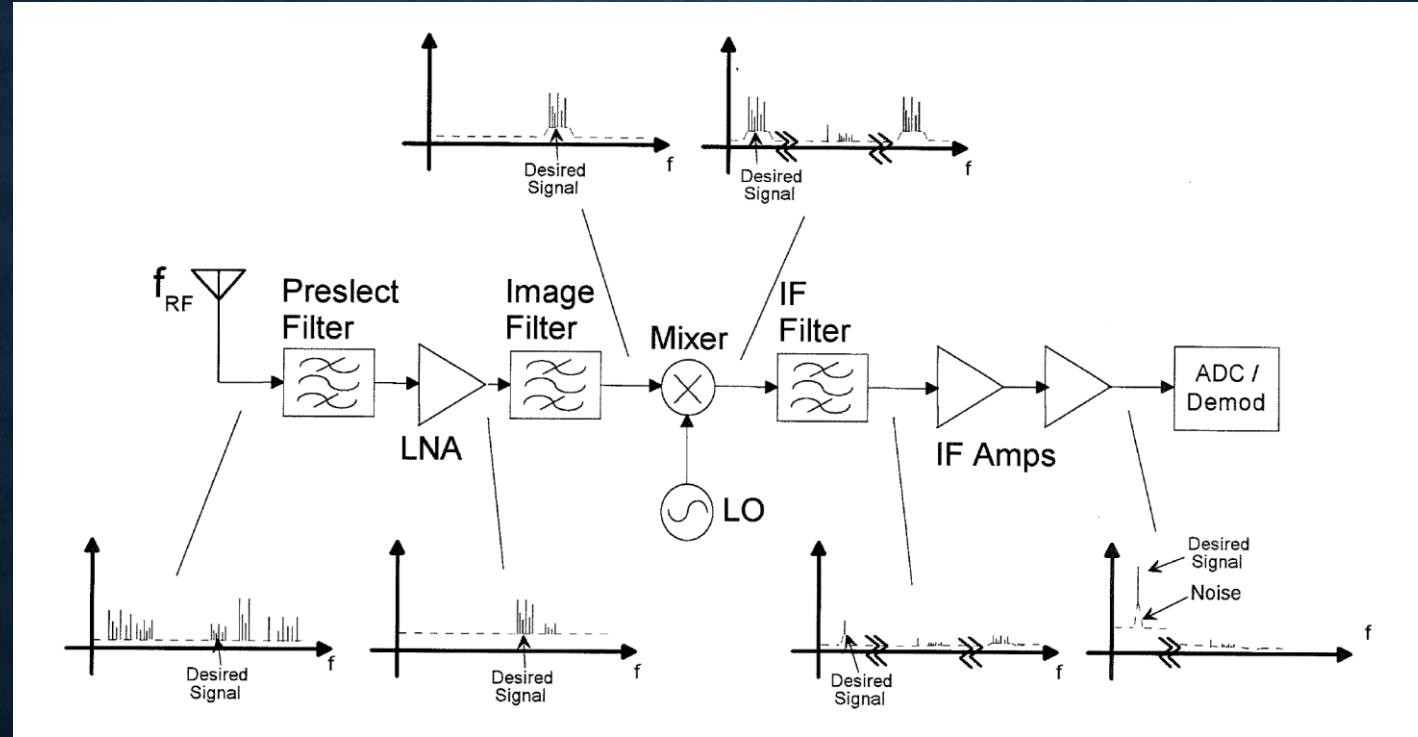

Passes entire “service band” to LNA and mixer




Blocking and Intermod Issues

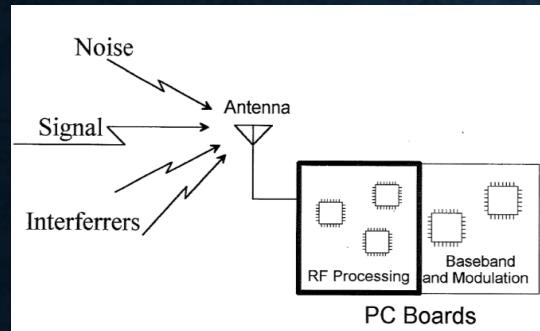

Strong interferers can overwhelm weak signals !

Blocking Problem

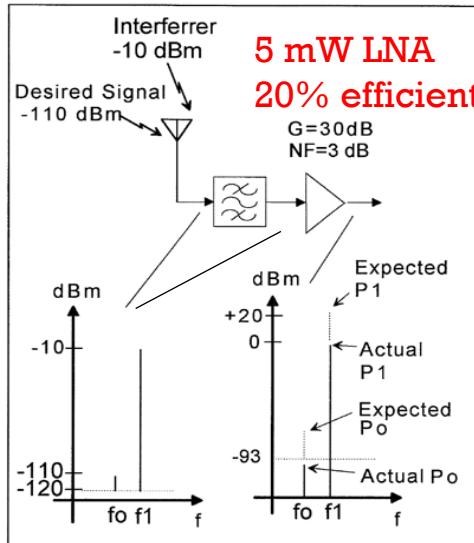

Effects

Gain compression
Desired signal below noise floor at output


Solutions

Use higher power LNA
Decrease LNA gain
Filter out f_1

NOTE

Could occur in later stages also **Like Mixer !!**

Intermod Problem

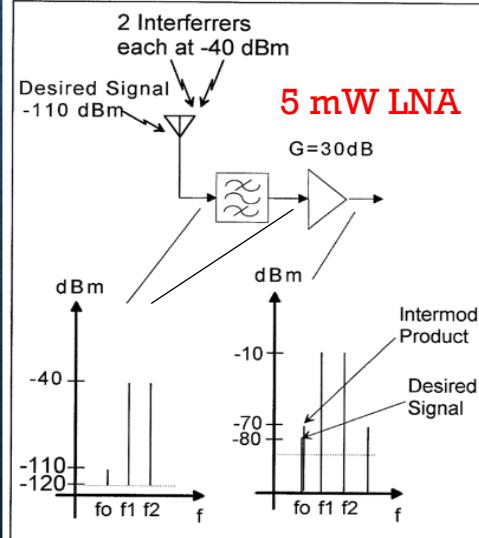

Effects

LNA generates "intermod products" at $2f_2-f_1$ & $2f_1-f_2$. Product at $2f_1-f_2 = f_0$ overpowers desired signal.


Solutions

Use higher power LNA.
Decrease LNA gain.
Filter out f_1, f_2

NOTE

Could occur in later stages also (especially mixer.)


Receiver Sensitivity Limitations

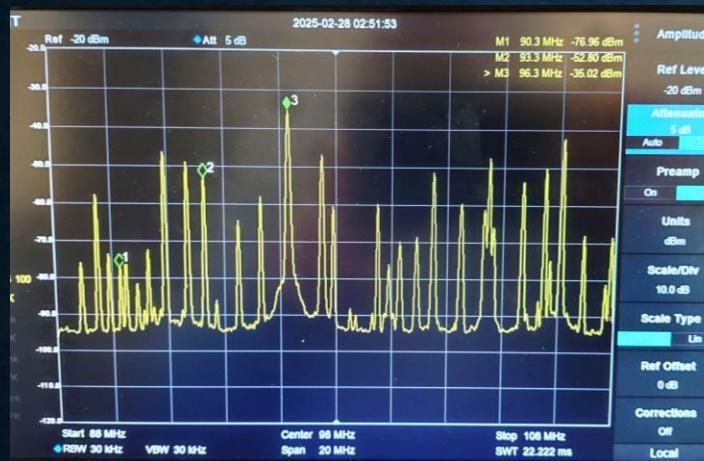

Typical receiver may miss half the available signals or more
(Car radios are better, depending on where they're parked)

Spectrum analyzer
Noise Figure = 30 dB !

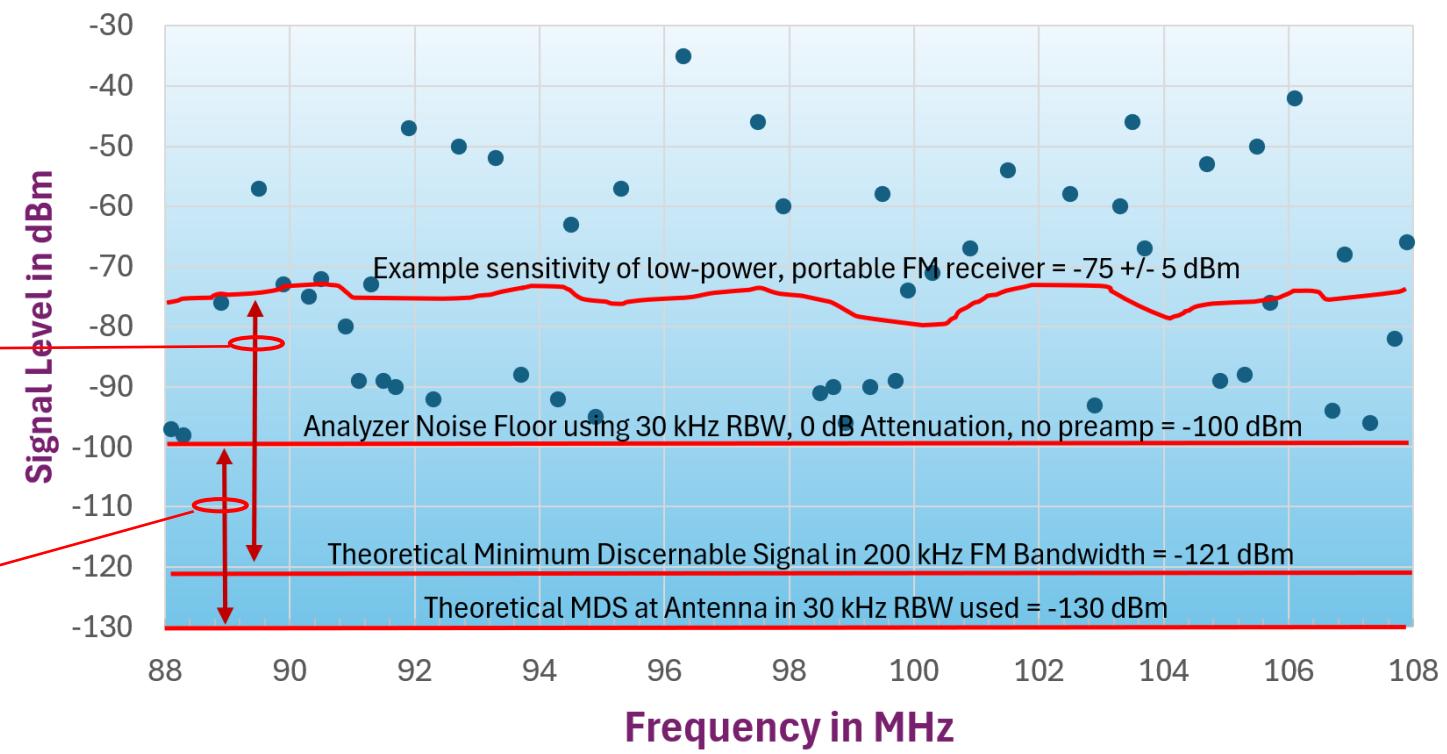FM Stations above -100 dBm near University
Using Outdoor Discone Antenna



Additional Receiver Architectures

Motivated mostly by “image” problems in down-conversion.
Still passes all (or most) of service band to LNA and mixer ☹

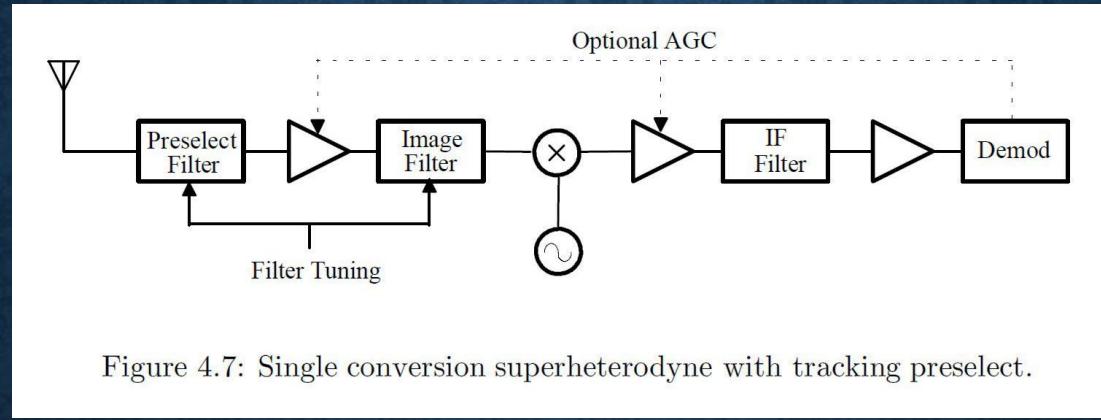


Figure 4.7: Single conversion superheterodyne with tracking preselect.

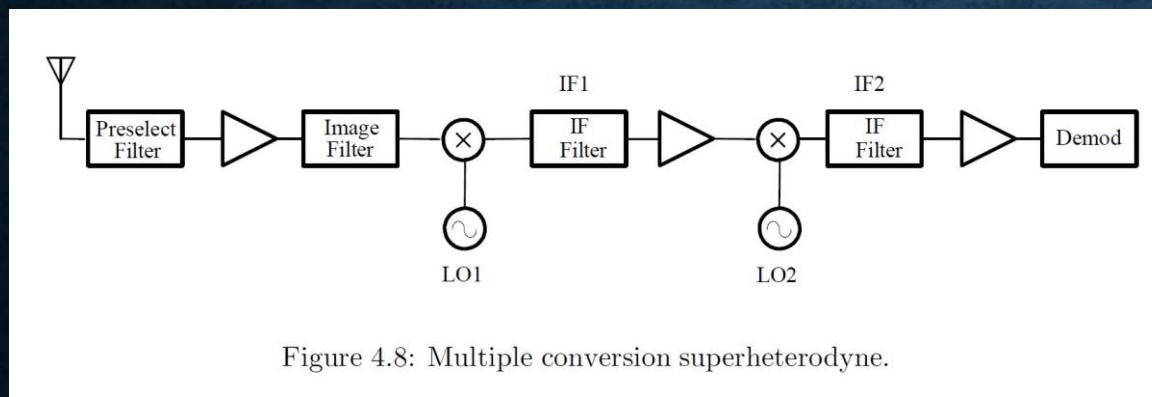


Figure 4.8: Multiple conversion superheterodyne.


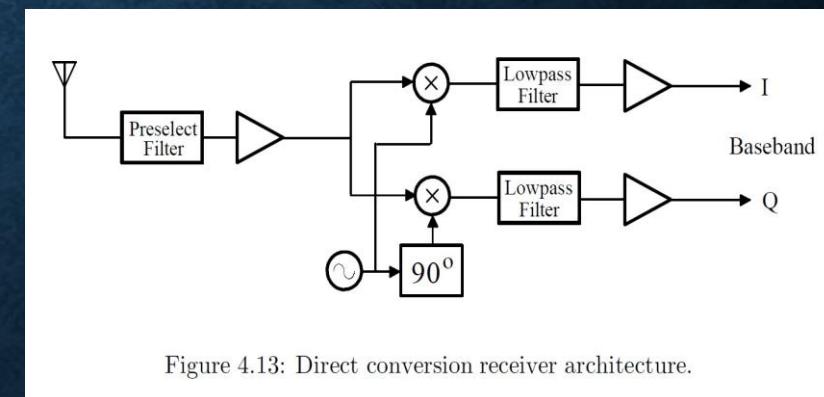


Figure 4.13: Direct conversion receiver architecture.

See Radio Design 101 video series, Epilogue 3

Ideal Low Power Receiver

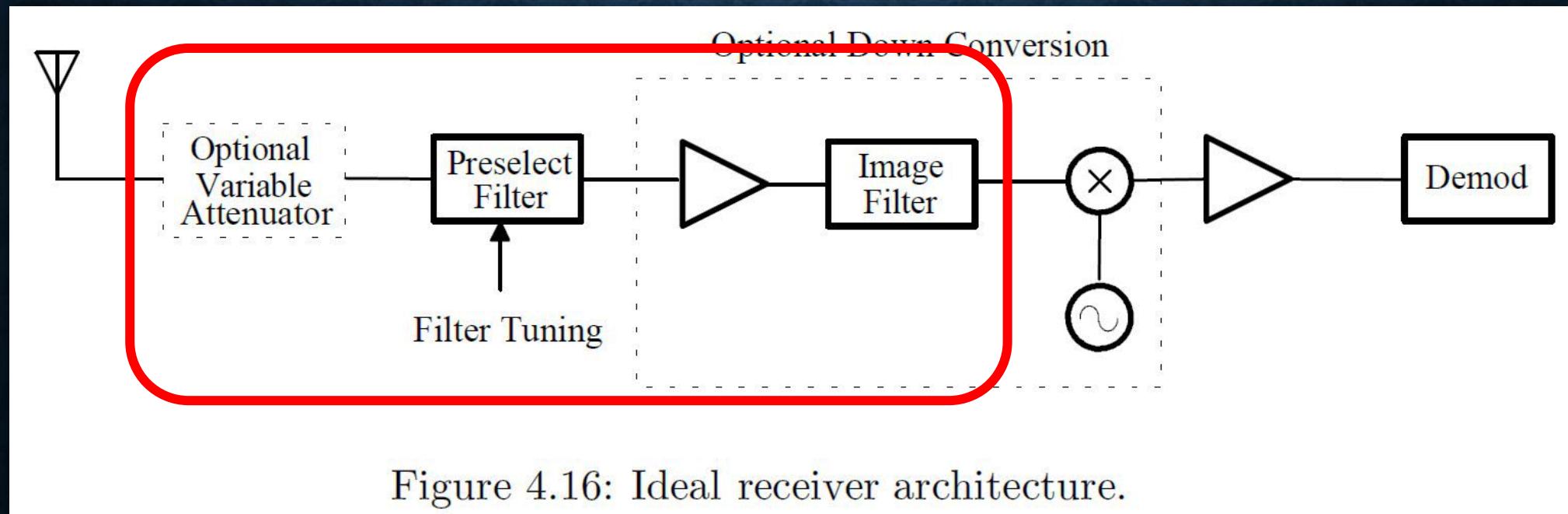Reduce Preselect Filter bandwidth to signal bandwidth !




From: “Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies”,
PhD dissertation, Virginia Tech, 1995

Today's Outline

- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- • *Circuit-level Solution Examples*
 - *Key Takeaways*
 - *Future Episodes in This Series*



Proposed Solution

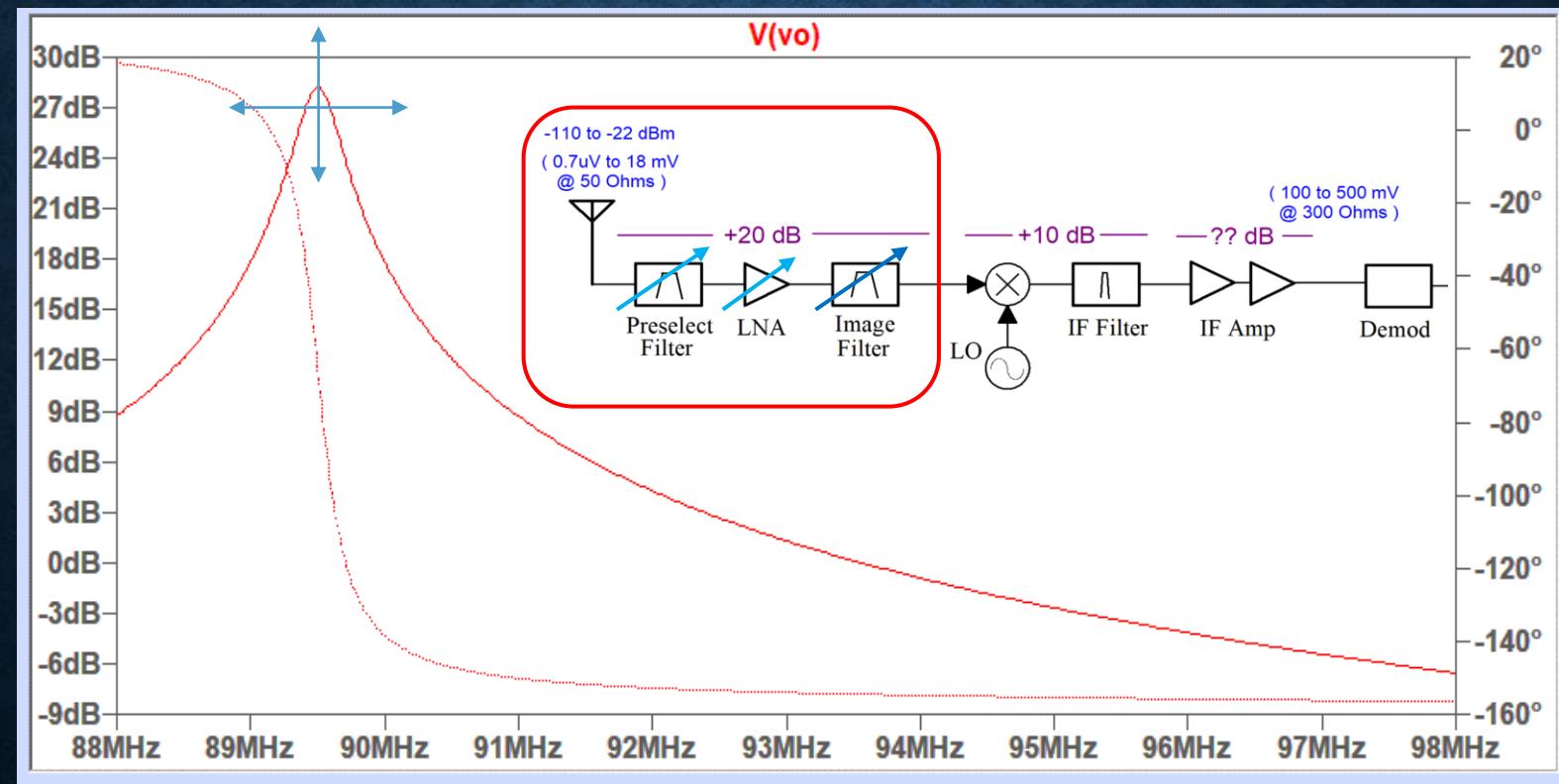*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Early Common-source Design 1

No Preselect Filtering ☹

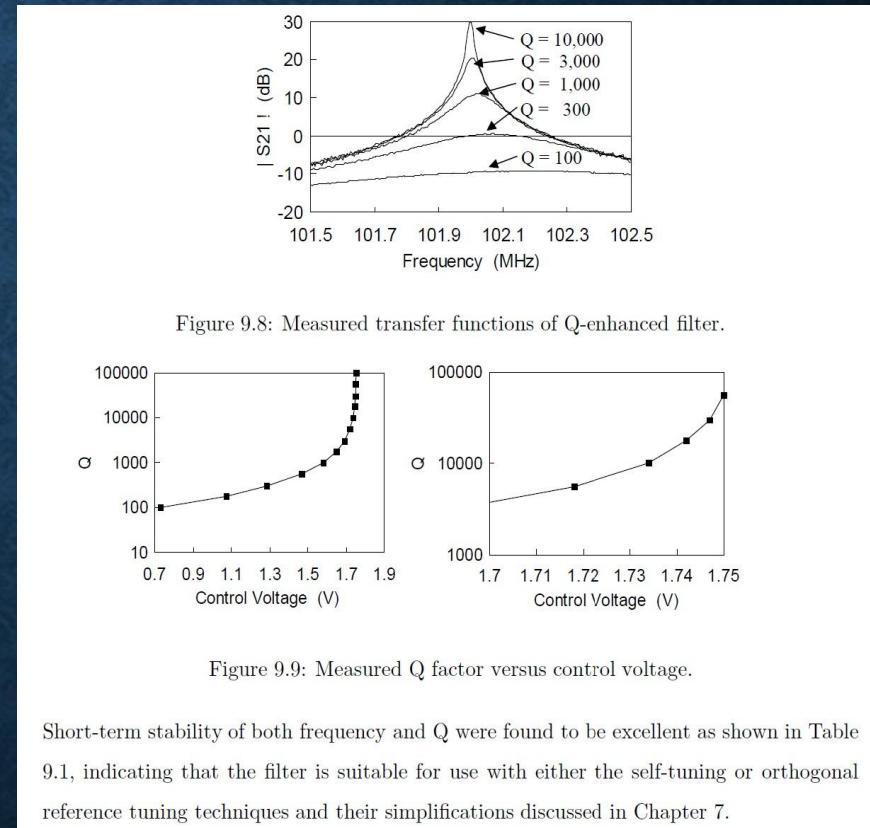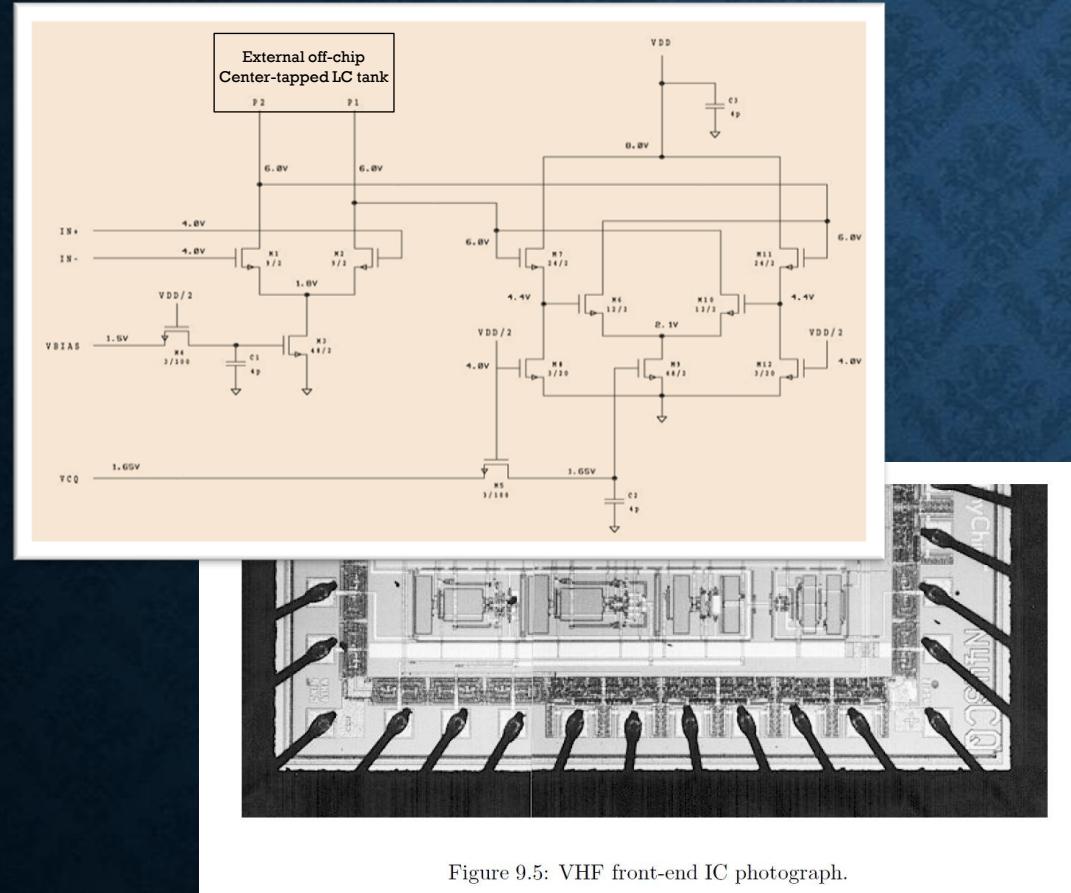

Short-term stability of both frequency and Q were found to be excellent as shown in Table 9.1, indicating that the filter is suitable for use with either the self-tuning or orthogonal reference tuning techniques and their simplifications discussed in Chapter 7.

From: “[Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies](#)”,
William B. Kuhn, PhD dissertation, Virginia Tech, 1995

Early 2-pole Design

For 200 MHz IF - No Preselect Filtering ☹

A photograph of the fabricated circuitry is shown in Figure 9.14. To provide minimum possible inductor coupling between the two identical second-order sections implemented on the die, the inductors were oriented diagonally opposite to each other. Chip area not used by the circuits discussed above was used to provide on-chip decoupling and supply bypass capacitors and to implement test structures. Total chip area for both second-order sections, excluding pads, is 3.3 mm².

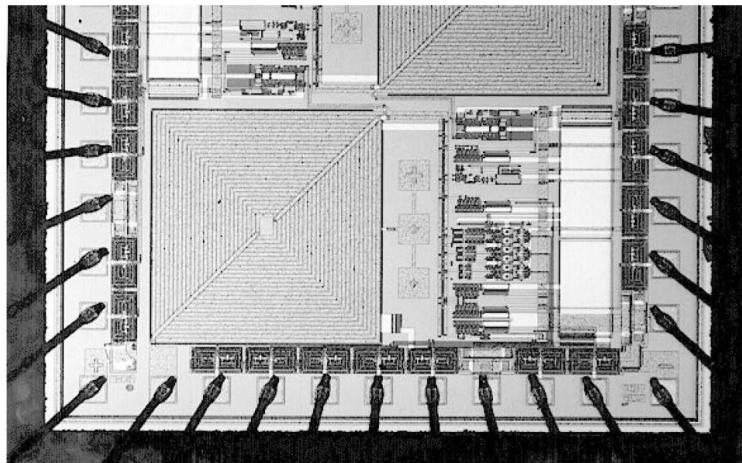


Figure 9.14: Photograph of chip layout.

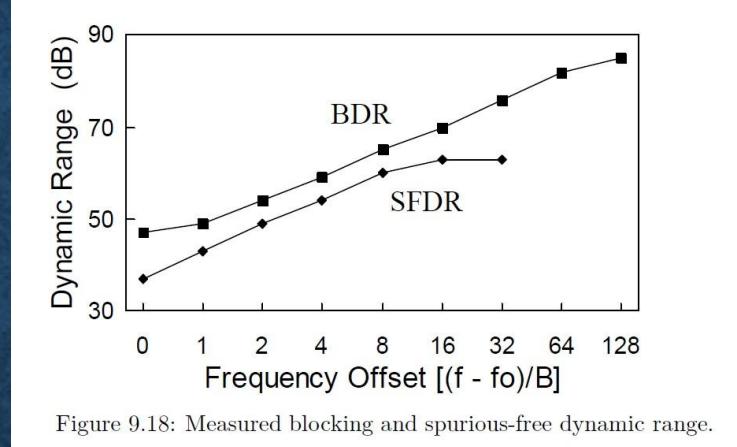


Figure 9.18: Measured blocking and spurious-free dynamic range.


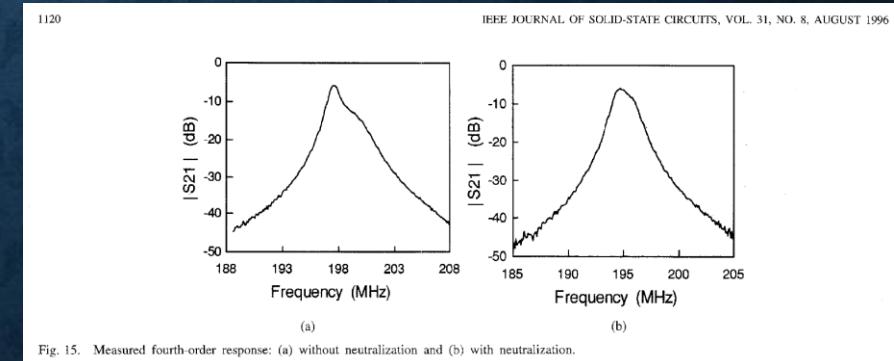
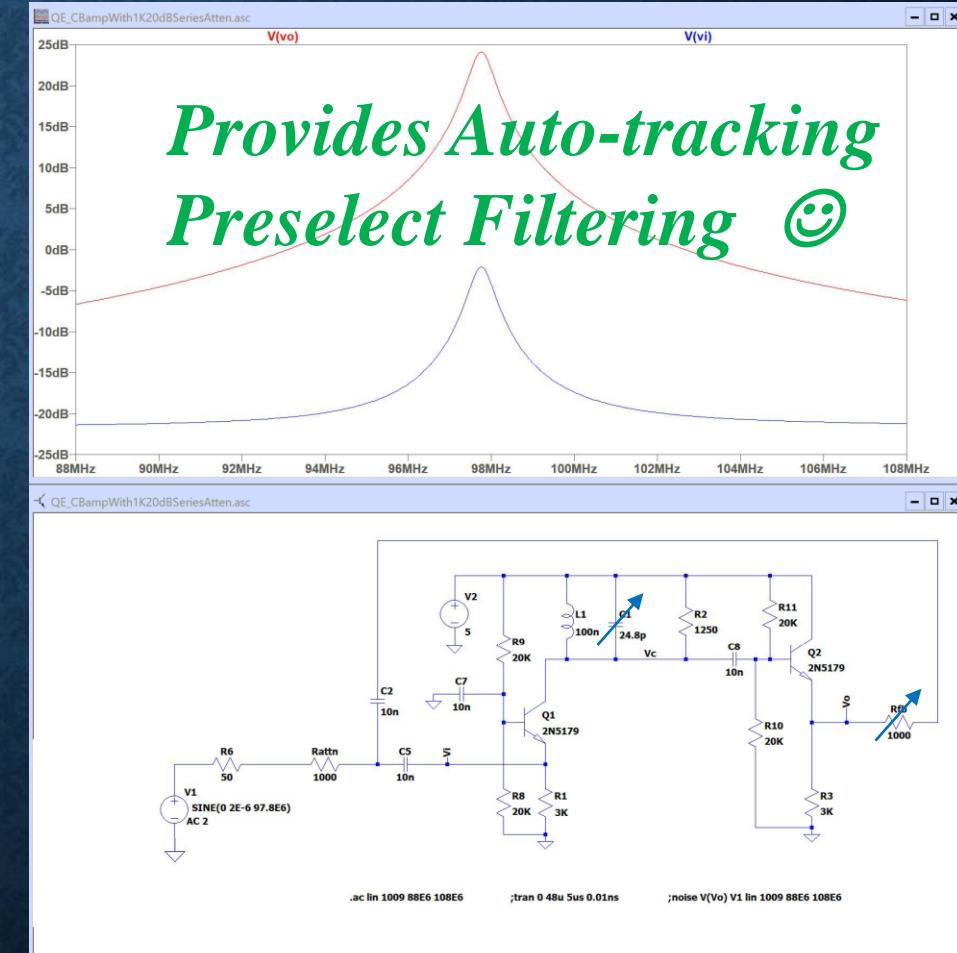


Fig. 15. Measured fourth order response: (a) without neutralization and (b) with neutralization.





From: "A 200 MHz CMOS Q-enhanced LC Bandpass Filter"

W B Kuhn, F W Stephenson, A Elshabini-Riad - IEEE Journal of Solid-State Circuits, 1996


Basic LNA vs New CB QE LNA

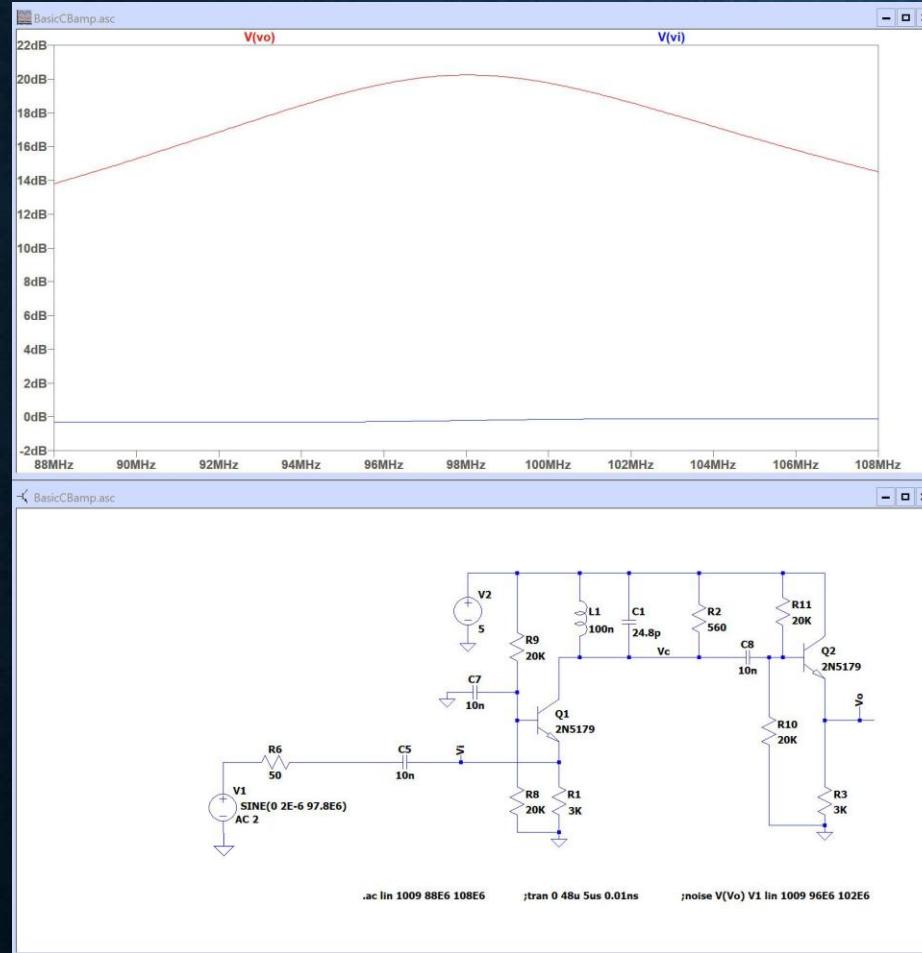

Basic LNA vs QE LNA Intermod Sims

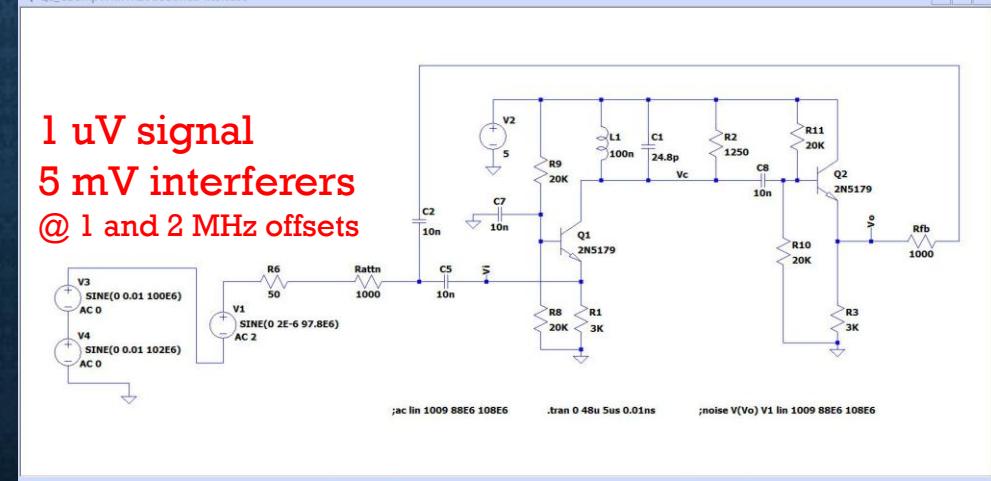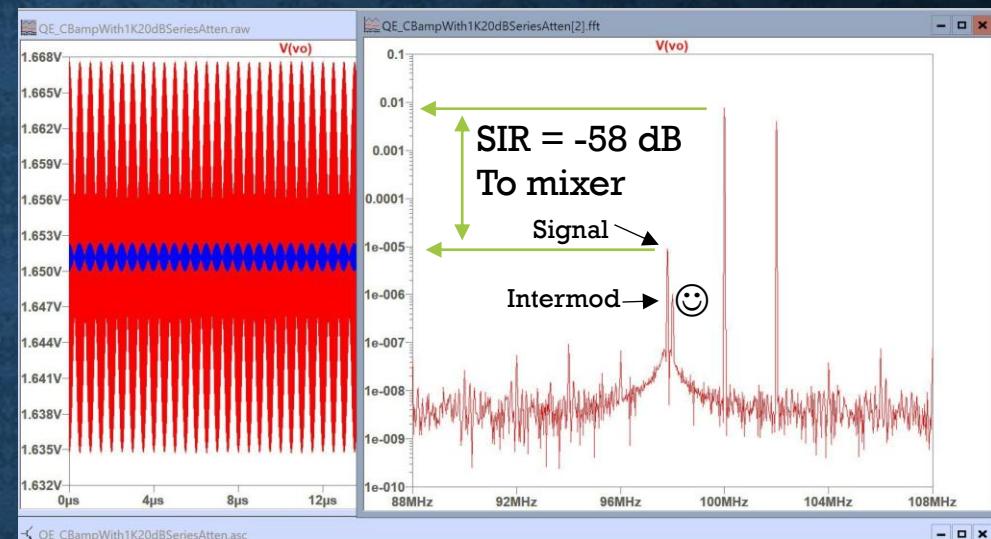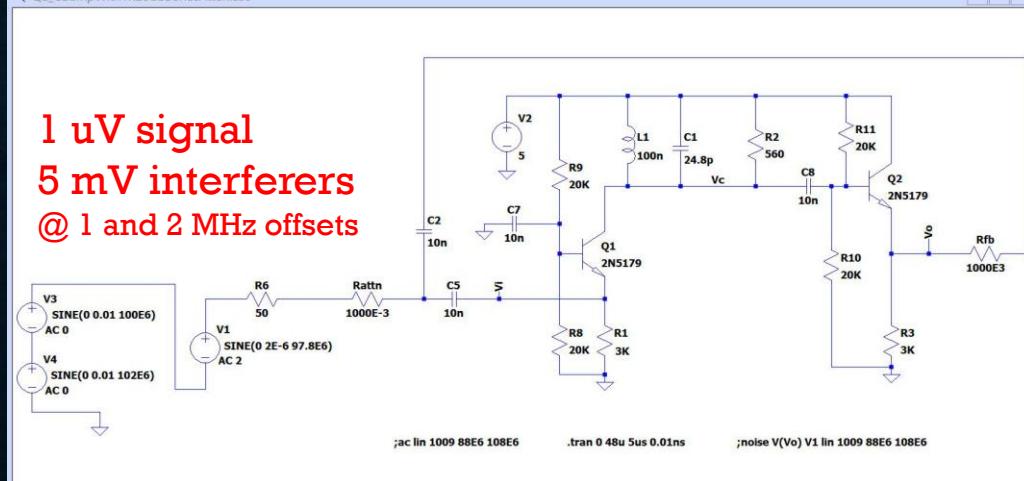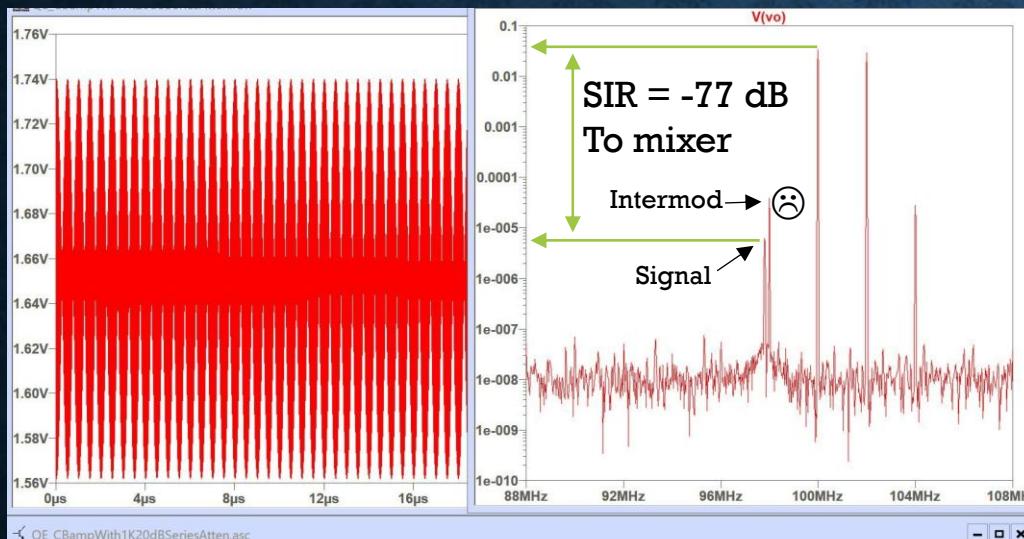


CB Q-enhanced Filter Prototype 2 (2023)

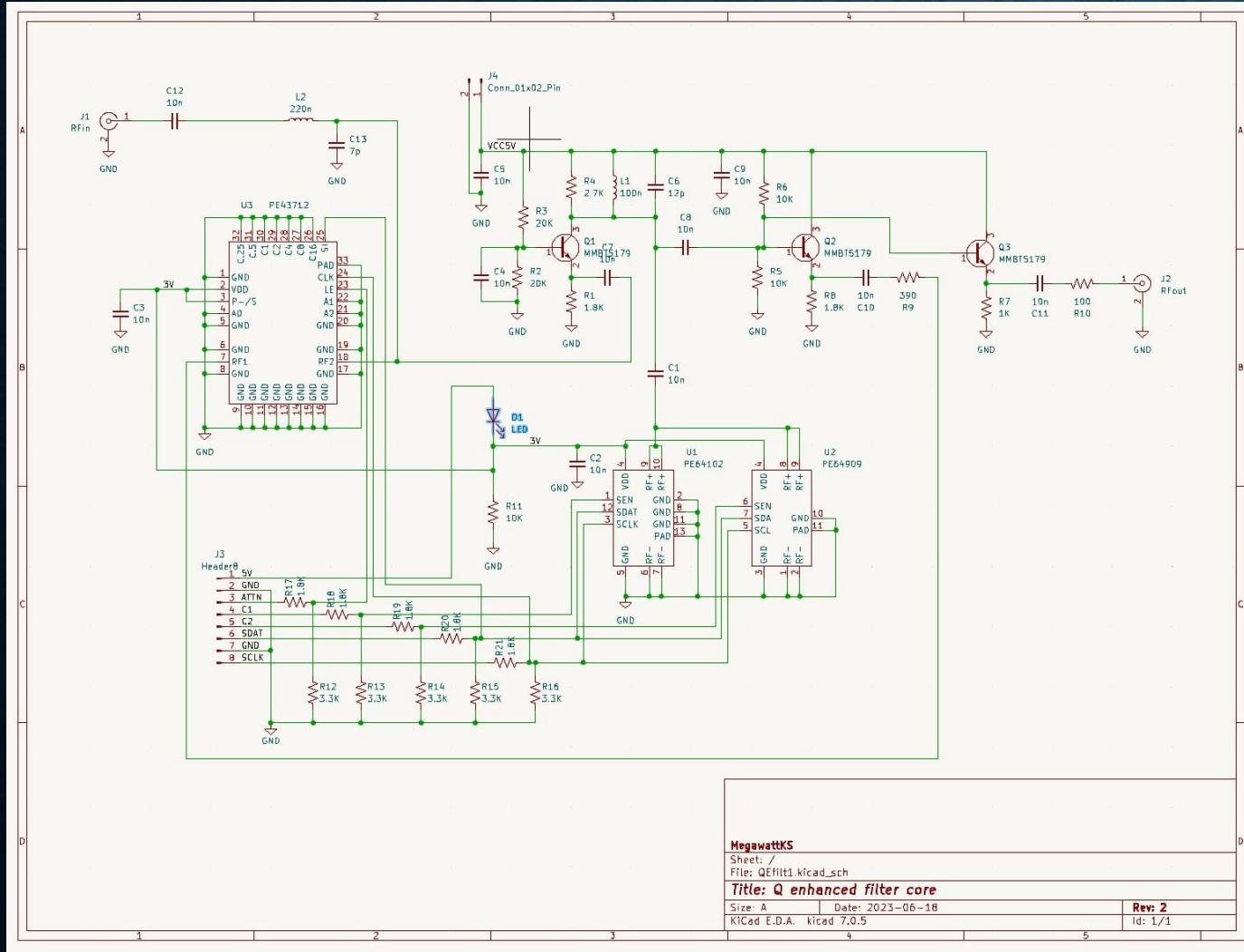

pSemi's DuNE™ technology enhancements deliver high linearity and exceptional harmonics performance. It is an innovative feature of the UltraCMOS® process, providing performance superior to GaAs with the economy and integration of conventional CMOS.


Figure 1. Functional Block Diagram

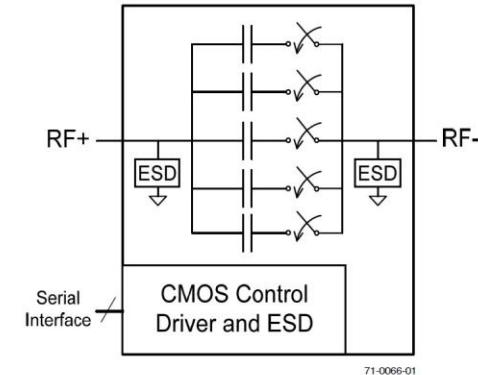


low current consumption
(typ. $I_D = 30 \mu\text{A} @ 2.8\text{V}$)

- Optimized for shunt configuration, but can also be used in series configuration
- Excellent 2 kV HBM ESD tolerance on all pins
- Applications include:
 - Antenna tuning
 - Tunable filters
 - Phase shifters


Figure 2. Package Type
12-lead 2 x 2 x 0.55 mm QFN

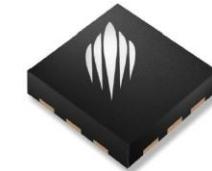
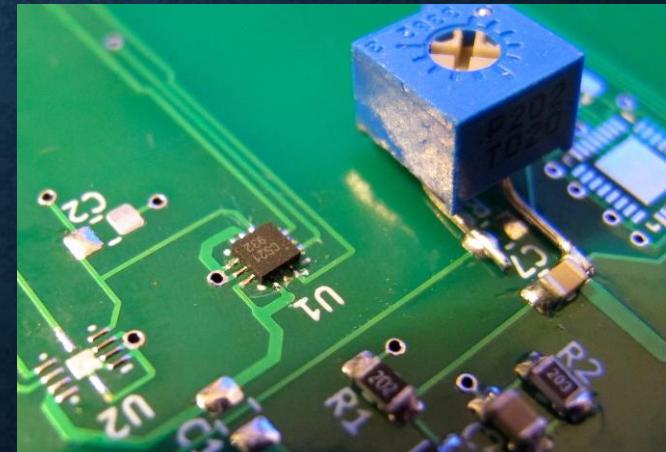
<https://www.psemi.com/pdf/datasheets/pe64102ds.pdf>



Digitally Controlled Tuning

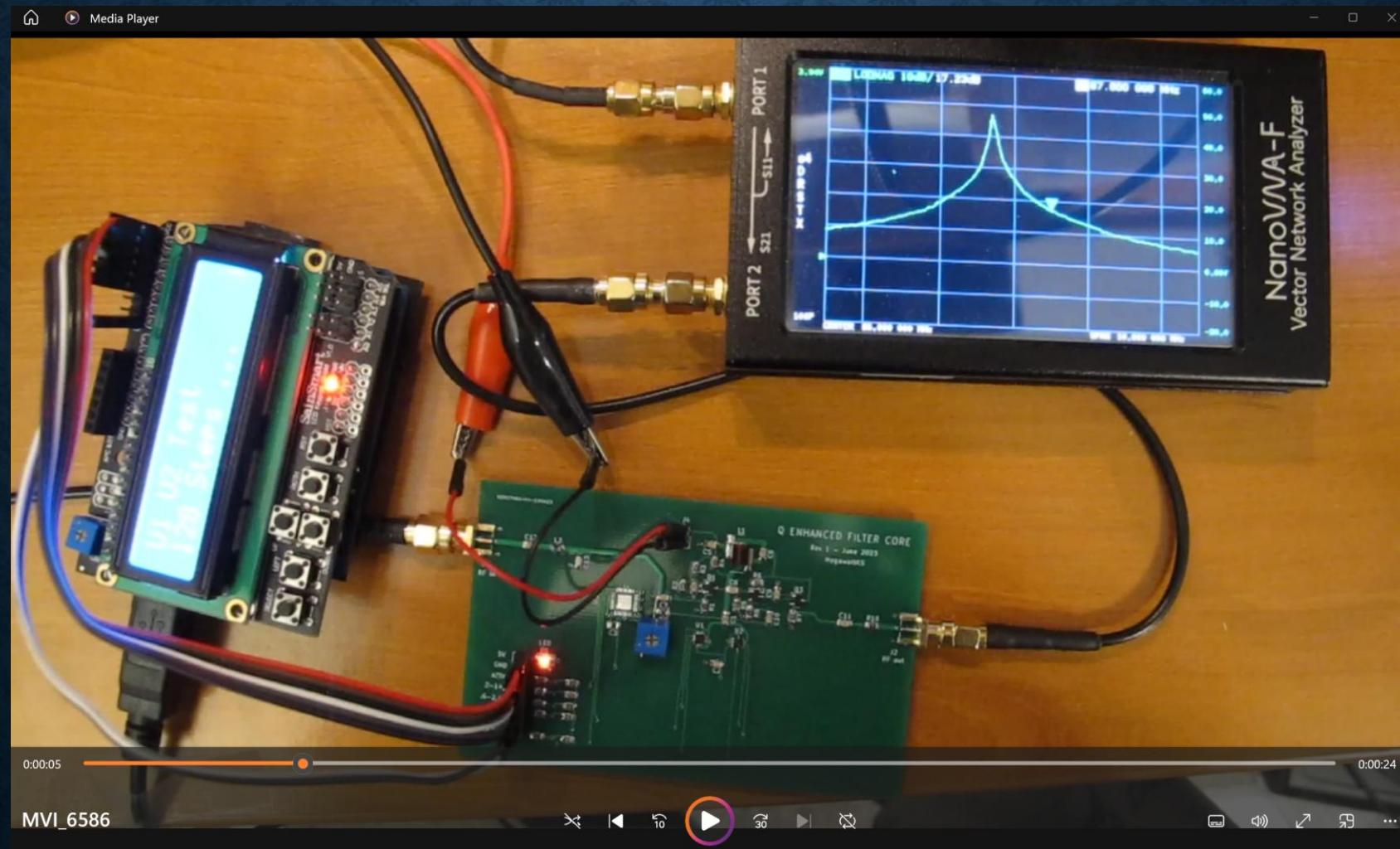

KIS Self-Tuning


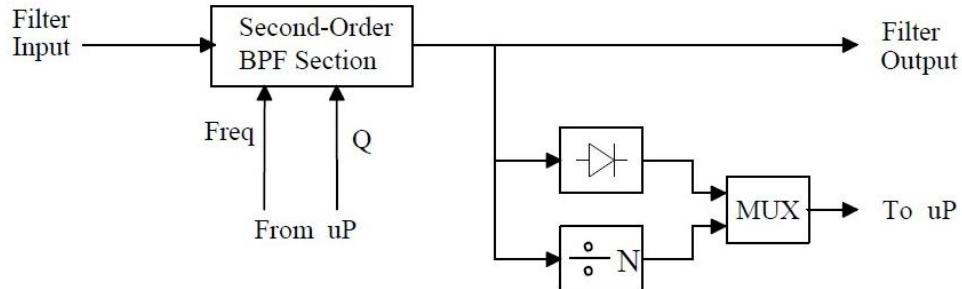
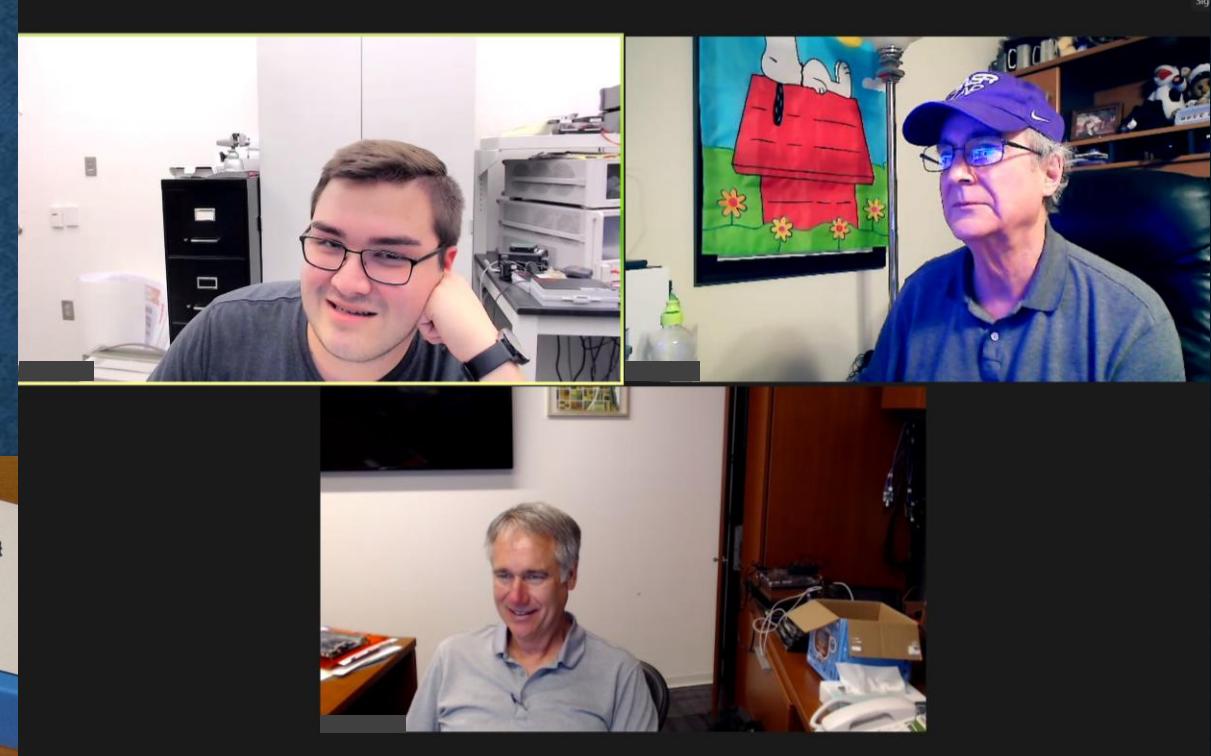
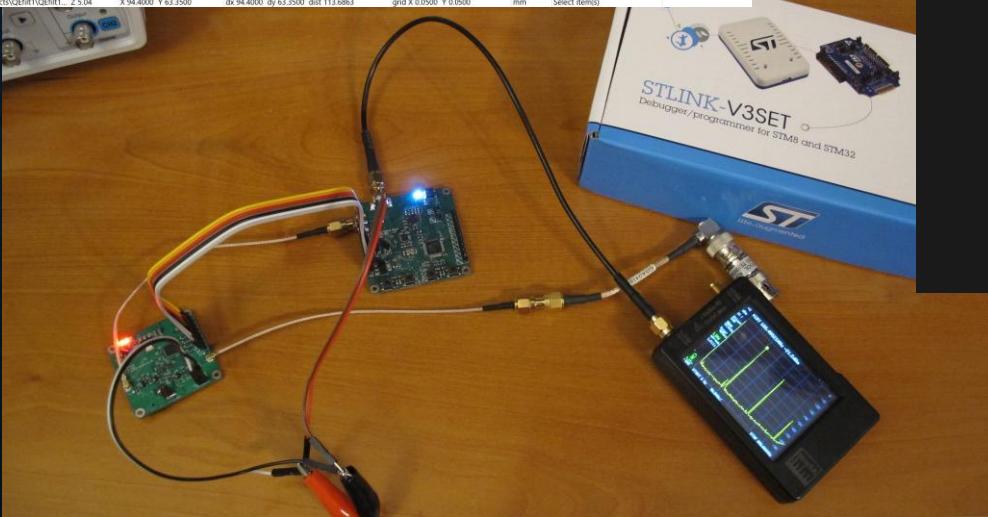


Figure 7.18: Self-tuning simplifications in superheterodyne receivers.

As before, filter frequency and Q control inputs are derived from the host receiver's microprocessor. However, measurement of frequency and Q is now performed using an amplitude detector and frequency prescaler incorporated into the filter die. Periodically, the filter is taken off-line and the Q is increased until the amplitude detector indicates that oscillation is present. The frequency of oscillation is then measured by the microprocessor's built-in

Recent Prototyping

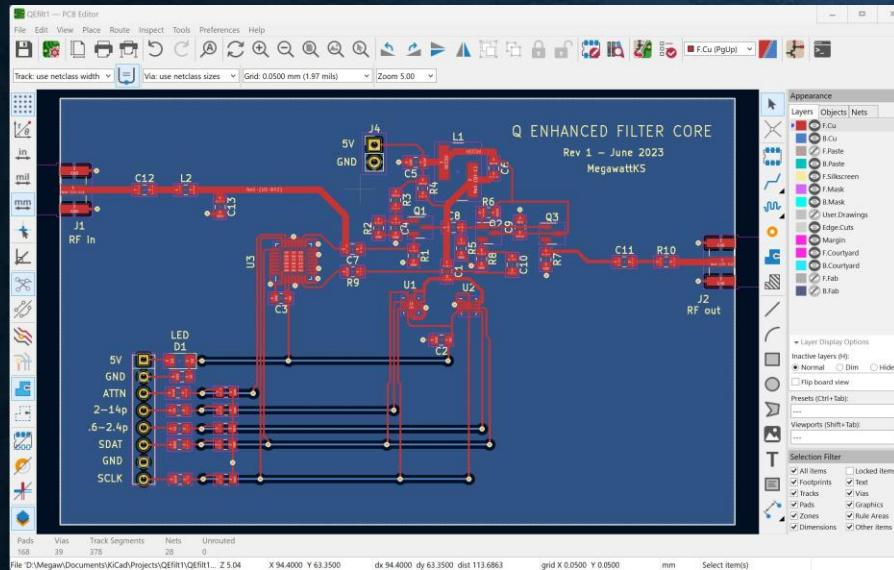

Today's Outline



- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- ✓ • *Circuit-level Solution Examples*
- • *Key Takeaways*
- *Future Episodes in This Series*

Key Takeaways from Episode 1

- Strong-signals can create blocking and intermod problems in existing receivers (**from in-band interferers**)
- Traditional solutions
 - Preselect (and image) filtering – Fixed bandwidth or (low-Q) tracking preselect architecture
 - Use RF (and IF) gain control and/or attenuators/AGC (trades noise figure for intermod mitigation)
 - Selective antennas (Directional and/or high-Q resonant)
 - **Burn more power in LNA and mixer !**


High-Power HF Radio Receiver Circuits

Icom 735 HF Transceiver

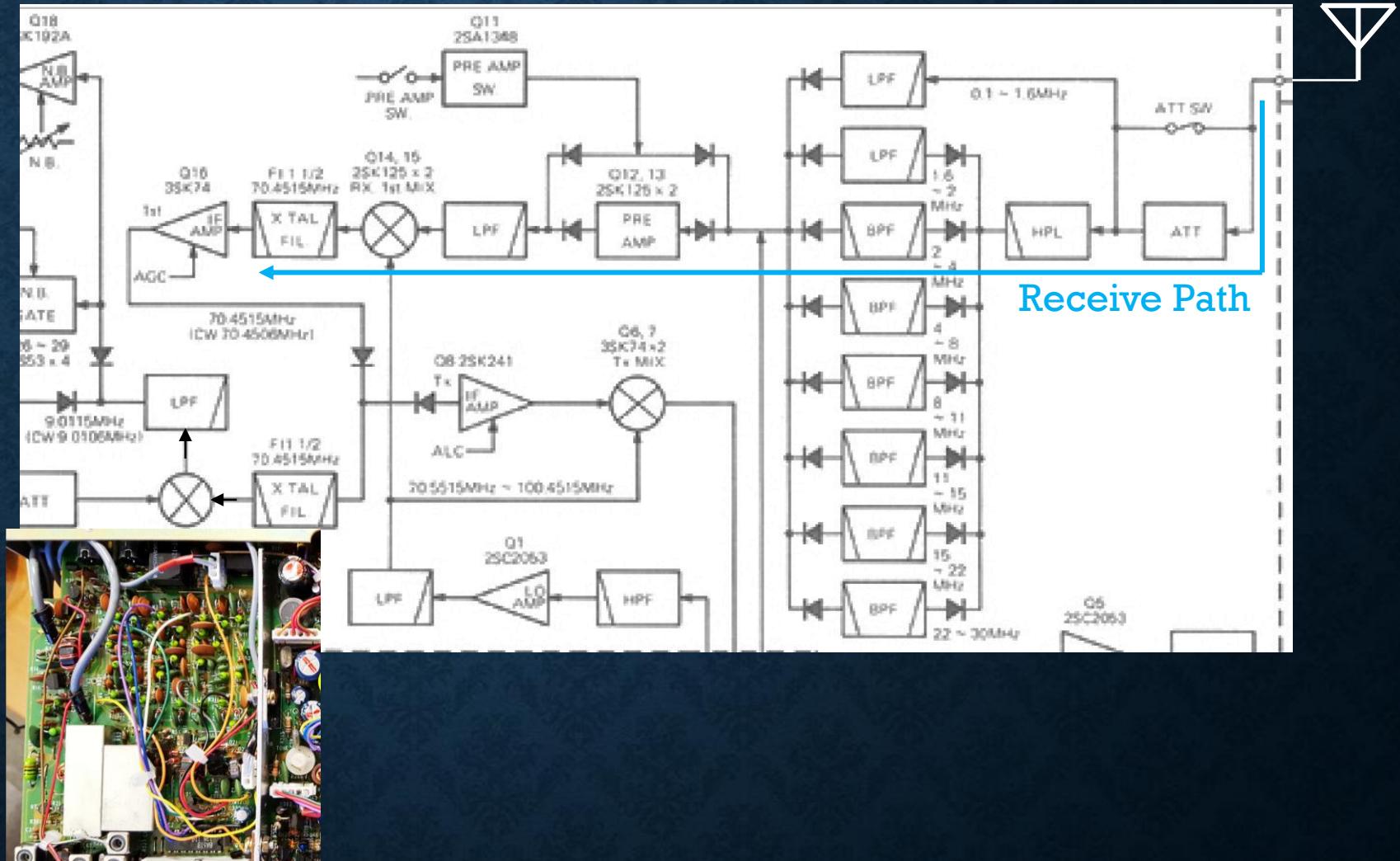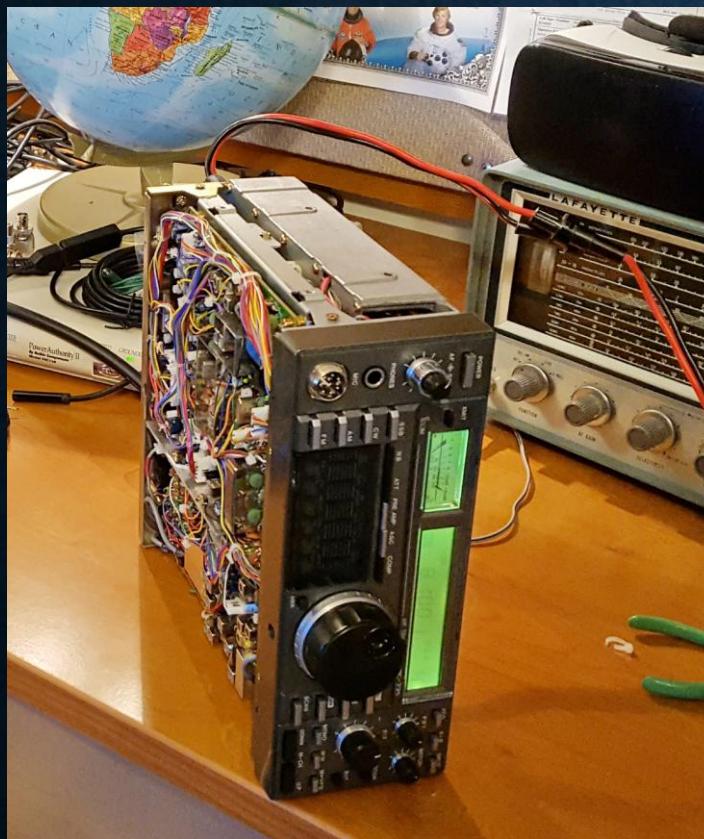

(See: <https://www.rigpix.com/icom/ic735.htm>)


High-Power HF Receiver Circuits

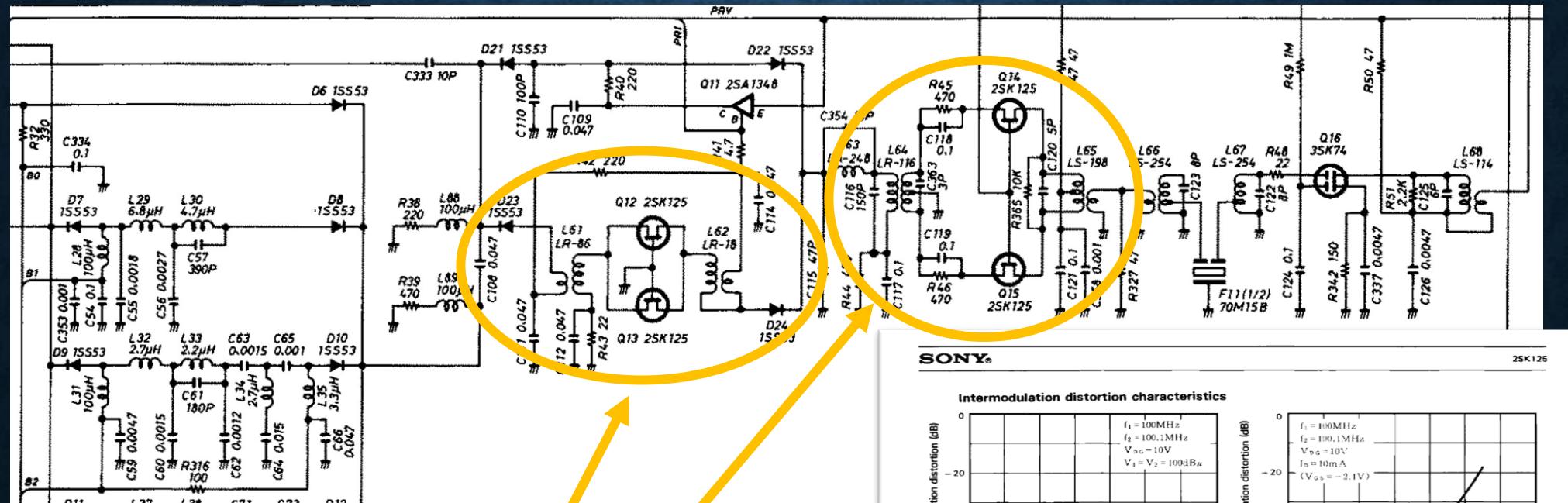

High Power (1/2 Watt) LNA

High Power (1/2 Watt) Mixer
(upconversion to 70 MHz)

2SK125 FET Intermod Characteristics

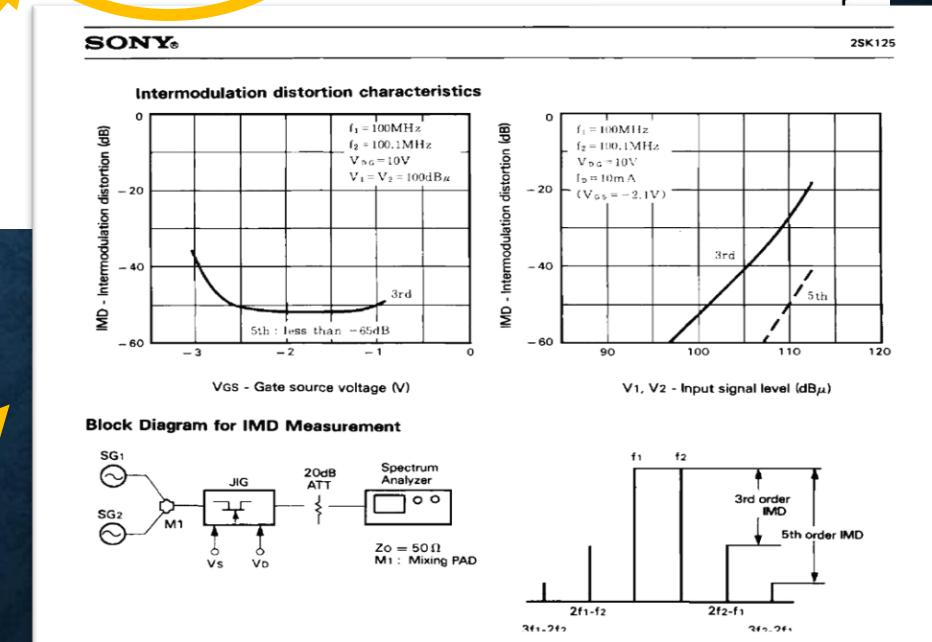


Key Takeaways (continued)

- Leveraging vintage technique of regeneration (positive feedback) in common-base form, using modern uP control (Q-enhanced filtering) is an easy way to make a significantly improved (low power) LNA
- CB QE-filter LNA architecture provides channel-width pre-select filtering that automatically tracks LC tank image-reject filter tuning ☺
- Can reduce power consumption required in receiver significantly (e.g. 10x to 100x reduction for front-end) !
- Not a panacea (yet... ☺)

Proposed Low Power Solution

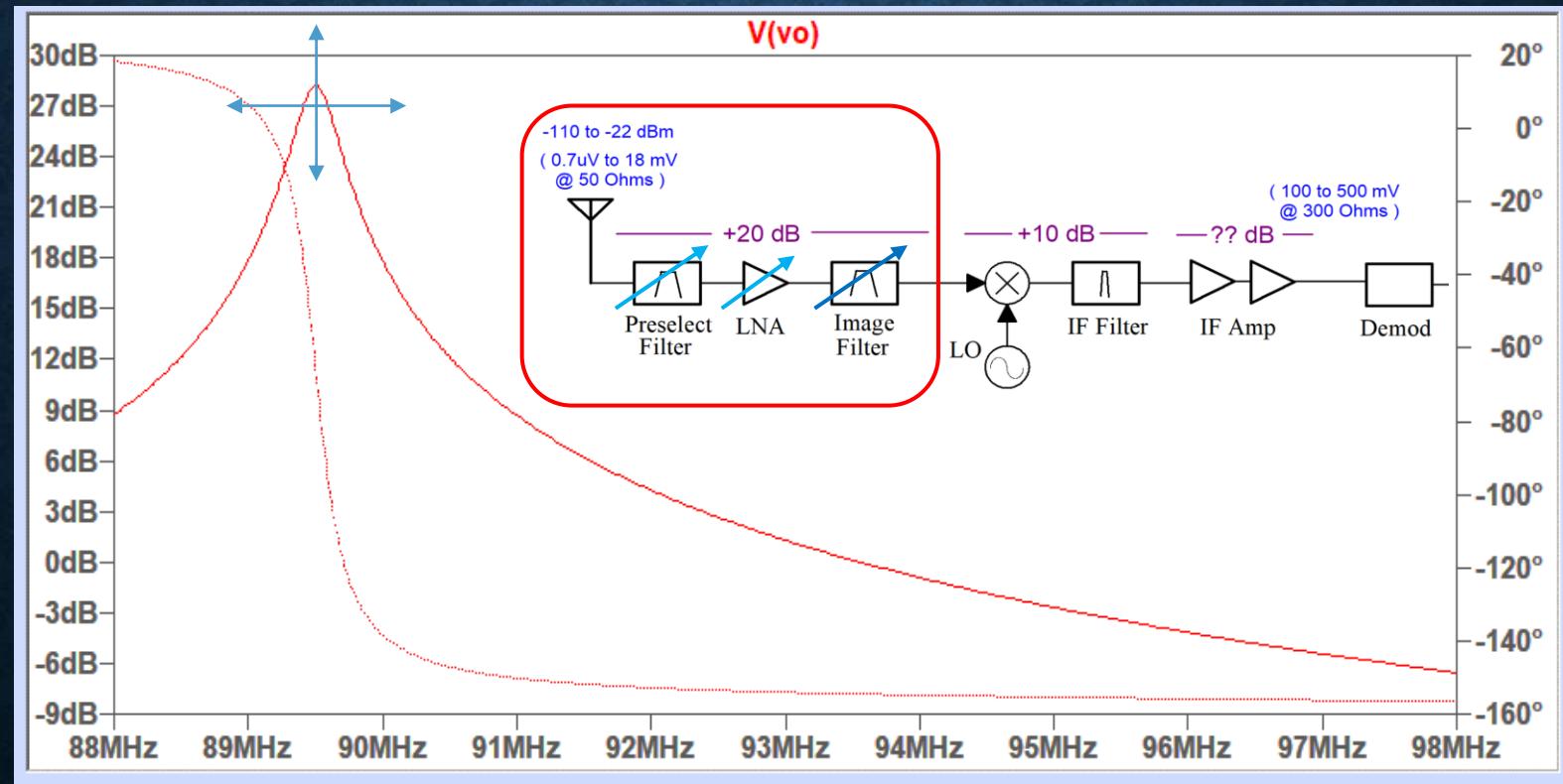*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Limitations and Alternatives

- Filter response of current design is only “one-pole”
- It’s still partly an active filter - but superior to earlier types, and traditional LNA designs
- Requires real-time tuning
- A (tunable, very-high-Q) electro-mechanical/acoustic design might be superior, if possible and sufficiently small (MEMs anyone?), and low cost
- **Always remember :** Antenna is also a very important part of the receiver system, and using attenuators can also work wonders !

Today's Outline

- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- ✓ • *Circuit-level Solution Examples*
- ✓ • *Key Takeaways*
- • *Future Episodes in This Series*

Possible Future Videos

- *Receiver Performance Measures (the math)*
 - *Compression, Intermodulation and 3rd Order Intercept Point*
 - *Noise Figure and Tradeoffs with Intermod Performance*
- *Design and simulation of common-base Q-enhanced Filters*
- *Self-tuning hardware and software*
- *Effects of LED lighting, switch-mode power-supplies, and general EMC on actual system noise floor and receiver sensitivity*

Thanks For Watching !

For research publications, please cite:

<https://www.youtube.com/user/MegawattKS>

<https://ecef files.org>

or specific sub-pages/publication/video

Thanks !